
Computer System Architecture

DR. Howida Youssry

Arithmetic Microoperations

A Microoperation is an elementary operation performed with the data stored in registers.

Usually, it consist of the following 4 categories:

- Register transfer: transfer data from one register to another
- Arithmetic microoperation
- Logic microoperation
- Shift microoperation

Arithmetic Microoperations

Symbolic designation	Description
$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow \overline{R2}$	Complement the contents of R2 (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's Complement the contents of R2 (negate)
$R3 \leftarrow R1 + \overline{R2} + 1$	R1 plus the 2's complement of R2 (subtract)
$R1 \leftarrow R1 + 1$	Increment the contents of R1 by one
$R1 \leftarrow R1 - 1$	Decrement the contents of R1 by one

Multiplication and division are not **basic** arithmetic operations

Multiplication : $R0 = R1 * R2$


Division : $R0 = R1 / R2$

Arithmetic Microoperations

- A single circuit does both arithmetic addition and subtraction depending on control signals.
- ● **Arithmetic addition:**
- $R3 \leftarrow R1 + R2$ (Here + is not logical OR. It denotes addition)

Binary Adder

 - To implement add microoperation with a n -bit binary adder:
 - n full adders connected in cascade, with
 - the output carry from each full adder connected to the input carry of the next full adder in chain




Arithmetic Microoperations


- **Arithmetic subtraction:**
- $R3 \leftarrow R1 + R2' + 1$
- where $R2'$ is the 1's complement of $R2$.
- Adding 1 to the one's complement is equivalent to taking the 2's complement of $R2$ and adding it to $R1$.

Binary Adder-Subtractor

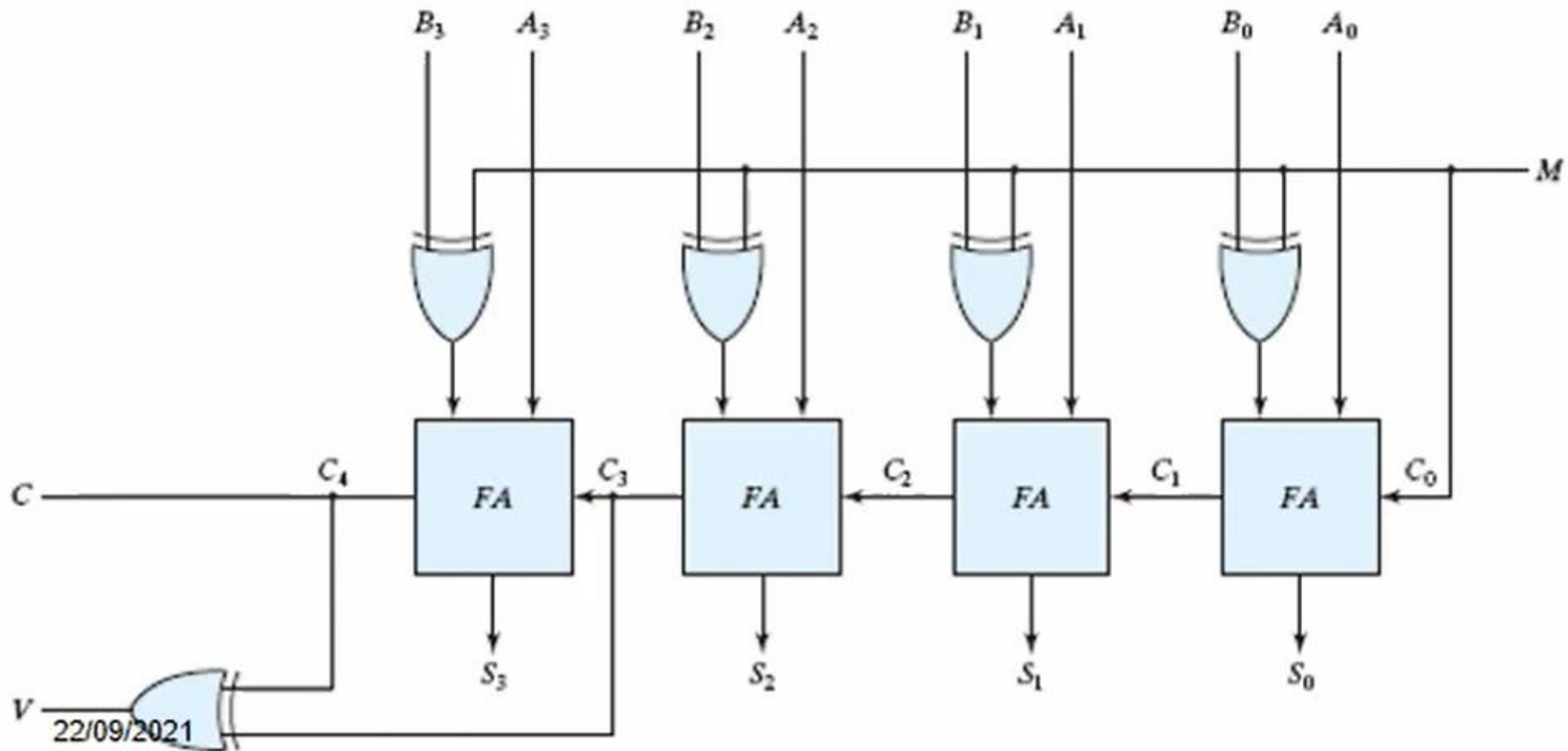- $M=0 \rightarrow$ Adder $(B \oplus 0 = B \text{ and } C_0=0)$
- $M=1 \rightarrow$ Subtractor $(B \oplus 1 = B' \text{ and } C_0=1)$



Binary Incrementor

 


4-bit Binary Incrementer

BINARY ADDER-SUBTRACTOR


- • $M = 0$: Note that $B \text{ XOR } 0 = B$. This is exactly the same as the binary adder with carry in $C_0 = 0$.
- $M = 1$: Note that $B \text{ XOR } 1 = B'$ (flip all B bits). The outputs of the XOR gates are thus the 1's complement of B.
- $M = 1$ also provides a carry in 1. The entire operation is: $A + B' + 1$.

Arithmetic Circuit

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

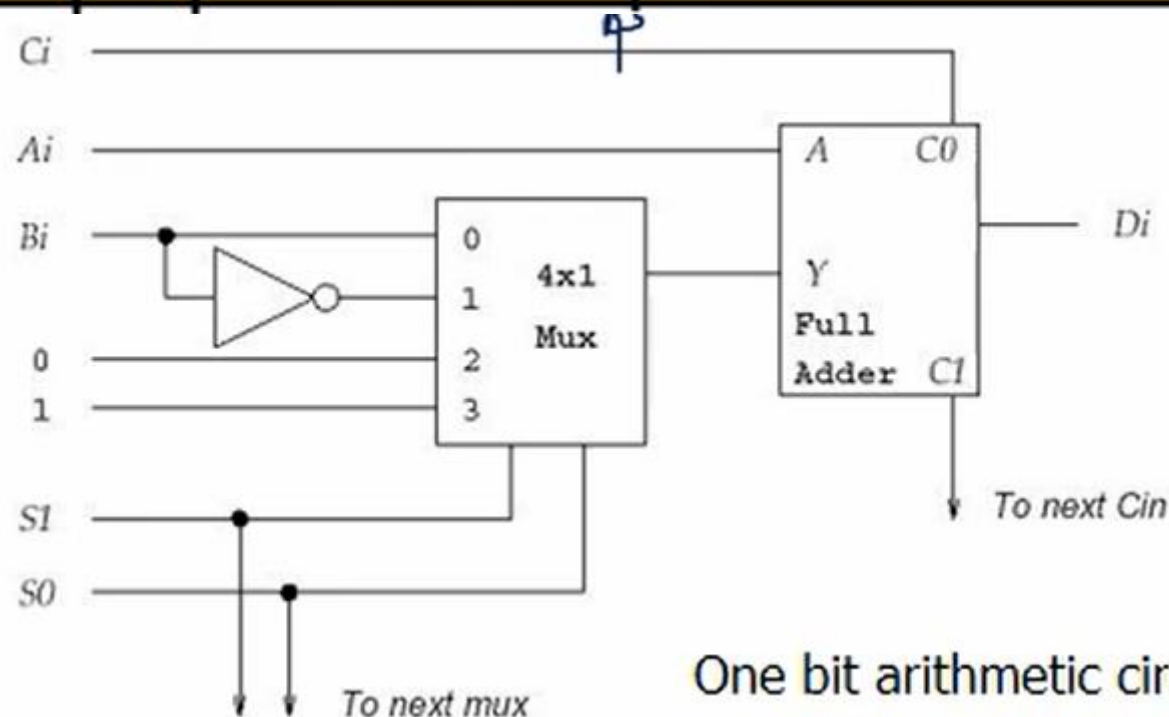

One bit arithmetic circuit

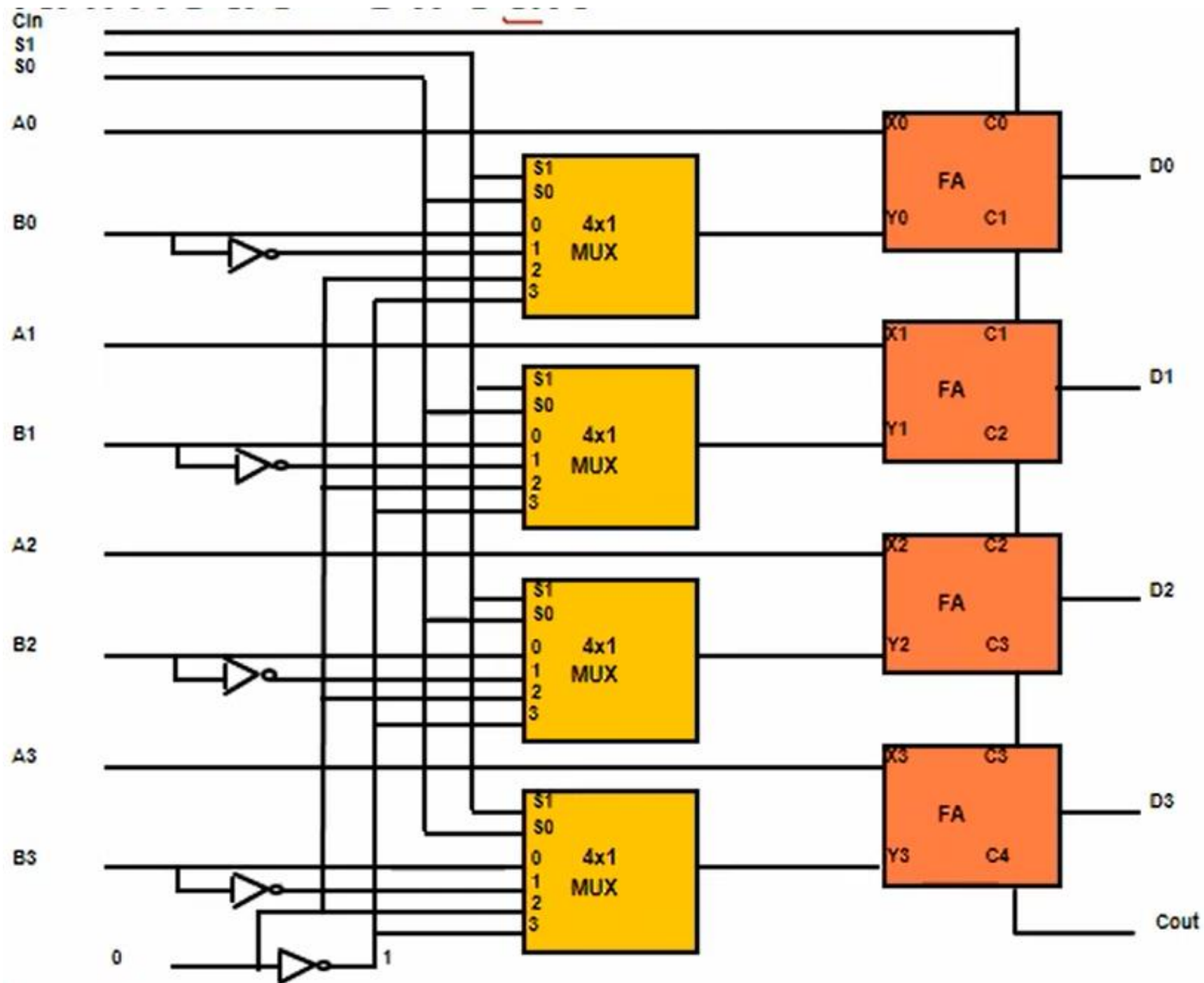

Logic Microoperations

- Logic microoperations consider *each bit of the register separately* and treat them as binary variables

$$P : R1 \leftarrow R1 \oplus R2$$

$$\begin{array}{rcl} 1010 & \text{Content of R1} & \\ + 1100 & \text{Content of R2} & \\ \hline 0110 & \text{Content of R1 after P=1} & \end{array}$$

- Manipulating the **bits** stored in a register

Symbolic designation	Description
$R0 \leftarrow \overline{R1}$	Logical bitwise NOT (1's complement)
$R0 \leftarrow R1 \wedge R2$	Logical bitwise AND (clears bits)
$R0 \leftarrow R1 \vee R2$	Logical bitwise OR (sets bits)
$R0 \leftarrow R1 \oplus R2$	Logical bitwise XOR (complements bits)

Logic Microoperations

- Logic microoperations consider *each bit of the register separately* and treat them as binary variables


$P: R1 \leftarrow R1 \oplus R2$

1010	Content of R1
+ 1100	Content of R2
<hr/>	
0110	Content of R1 after P=1

Special Symbols

- \vee Used for denote OR
- \wedge Used for denote AND

Example:

 

More Logic Microoperation

X	Y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1


TABLE 4-5. Truth Table for 16 Functions of Two Variables

Boolean function	Microoperation	Name	Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear	$F_8 = (x+y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_1 = xy$	$F \leftarrow A \wedge B$	AND	$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Ex-NOR
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$		$F_{10} = y'$	$F \leftarrow \overline{B}$	Compl-B
$F_3 = x$	$F \leftarrow A$	Transfer A	$F_{11} = x+y'$	$F \leftarrow A \vee \overline{B}$	
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$		$F_{12} = x'$	$F \leftarrow \overline{A}$	Compl-A
$F_5 = y$	$F \leftarrow B$	Transfer B	$F_{13} = x'+y$	$F \leftarrow \overline{A} \vee B$	
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Ex-OR	$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_7 = x+y$	$F \leftarrow A \vee B$	OR	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	set to all 1's

TABLE 4-6. Sixteen Logic Microoperations

HARDWARE IMPLEMENTATION OF LOGIC MICROOPERATIONS

 - However, most systems only implement four of these
 - AND (\wedge), OR (\vee), XOR (\oplus), Complement/NOT
- The others can be created from combination of these



S_1	S_0	E_i	Operation
0	0	$E = A \wedge B$	AND
0	1	$E = A \vee B$	OR
1	0	$E = A \oplus B$	XOR
1	1	$E = \bar{A}$	Complement

Function table

Some Applications

- Logic microoperations are very useful for *manipulating individual bits* or *a portion of a word* stored in a register
- Used to change bit values, delete a group of bits, or insert new bit values

Selective-set $A \leftarrow A \vee B$

- The selective-set operation sets to 1 the bits in register A where there are corresponding 1's in register B. It does not effect bit positions that have 0's in B

1010 A before

1100 B(Logic Operand)

1110 A After

Selective-set

Selective-complement $A \leftarrow A \oplus B$

» The selective-complement operation complements bits in A where there are corresponding 1's in B. It does not effect bit positions that have 0's in B

1010	A before
1100	B(Logic Operand)
<hr/>	
0110	A After

Selective-complement

Selective-clear $A \leftarrow A \wedge \overline{B}$

The selective-clear operation clears to 0 the bits in A only where there are corresponding 1's in B

1010 A before

1100 B(Logic Operand)

0010 A After

Selective-clear

Selective-mask $A \leftarrow A \wedge B$

The mask operation is similar to the selective-clear operation except that the bits of A are cleared only where there are corresponding 0's in B

1010 A before

0011 B(Logic Operand)

0010 A After

Selective-mask

Insert

The insert operation inserts a new value into a group of bits


This is done by first masking the bits and then ORing them with the required value

1) Mask

0110 1010 A before

0000 1111 B mask

0000 1010 A after mask

 

2) OR

0000 1010 A before

1001 0000 B insert

1001 1010 A after insert

Clear

0110 A

0110 B

0000 A after clear

Clear $A \leftarrow A \oplus B$

» The clear operation compares the words in A and B and produces an all 0's result if the two numbers are equal

Logic Microoperations


Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.

Example

- Extend the previous logic circuit to accommodate XNOR, NAND, NOR, and the complement of the second input.

S2	S1	S0	Output	Operation
0	0	0	$\mathbf{X \wedge Y}$	AND
0	0	1	$\mathbf{X \vee Y}$	OR
0	1	0	$\mathbf{X \oplus Y}$	XOR
0	1	1	$\overline{\mathbf{A}}$	Complement A
1	0	0	$\overline{(\mathbf{X \wedge Y})}$	NAND
1	0	1	$\overline{(\mathbf{X \vee Y})}$	NOR
1	1	0	$\overline{(\mathbf{X \oplus Y})}$	XNOR
1	1	1	$\overline{\mathbf{B}}$	Complement B

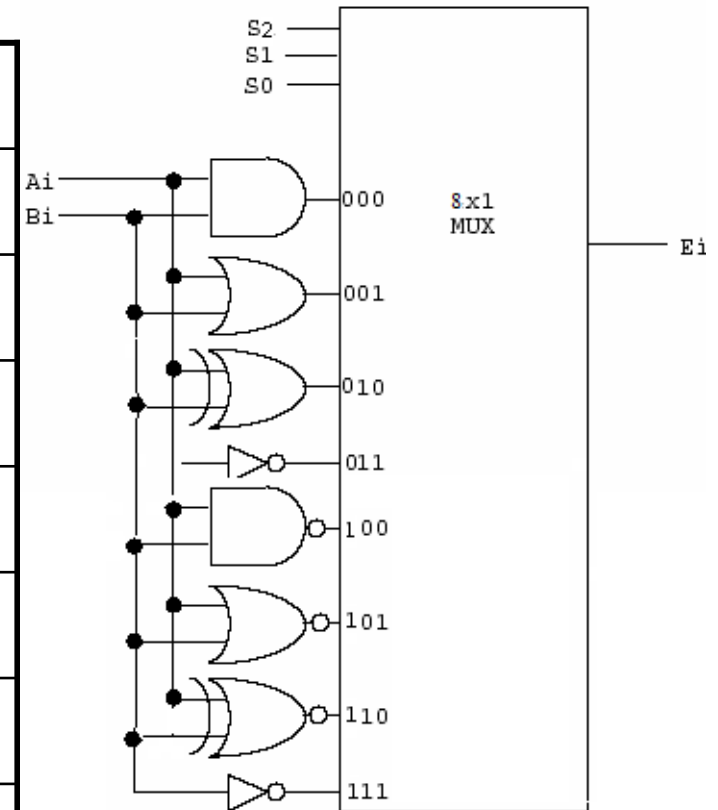

Homework 1

- Design a multiplexer to select one of the 16 functions.

Boolean function	Microoperation	Name	Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear	$F_8 = (x+y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_1 = xy$	$F \leftarrow A \wedge B$	AND	$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Ex-NOR
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$		$F_{10} = y'$	$F \leftarrow \overline{B}$	Compl-B
$F_3 = x$	$F \leftarrow A$	Transfer A	$F_{11} = x+y'$	$F \leftarrow A \vee \overline{B}$	
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$		$F_{12} = x'$	$F \leftarrow \overline{A}$	Compl-A
$F_5 = y$	$F \leftarrow B$	Transfer B	$F_{13} = x'+y$	$F \leftarrow \overline{A} \vee B$	
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Ex-OR	$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_7 = x+y$	$F \leftarrow A \vee B$	OR	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	set to all 1's

TABLE 4-6. Sixteen Logic Microoperations

Shift Microoperations

- Shift Microoperations :
 - Shift microoperations are used for serial transfer of data
 - Three types of shift microoperation : *Logical*, *Circular*, and *Arithmetic*

Shift Microoperations

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular shift-right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right R

TABLE 4-7. Shift Microoperations

Logical Shift

- A ***logical shift*** transfers 0 through the serial input
- The bit transferred to the end position through the serial input is assumed to be 0 during a logical shift (***Zero inserted***)

Logical Shift Example

1. **Logical shift:** Transfers 0 through the serial input.

R1 \leftarrow shl R1 Logical shift-left

R2 \leftarrow shr R2 Logical shift-right

(Example) Logical shift-left


10100011 \rightarrow 01000110

(Example) Logical shift-right

10100011 \rightarrow 01010001

R1 \leftarrow shl R1


R2 \leftarrow shr R2

 

Circular Shift

- The ***circular shift*** circulates the bits of the register around the two ends without loss of information

Circular shift-left

 

Circular Shift Example

Circular shift-left $R1 \leftarrow cil\ R1$

Circular shift-right $R2 \leftarrow cir\ R2$

(Example) Circular shift-left

10100011 is shifted to 01000111

(Example) Circular shift-right


10100011 is shifted to 11010001

Arithmetic Shift

- An ***arithmetic shift*** shifts a ***signed*** binary number to the left or right
- An arithmetic ***shift-left multiplies*** a signed binary number by 2
- An arithmetic ***shift-right divides*** the number by 2
- In arithmetic shifts the sign bit receives a special treatment

Arithmetic Shift Right

 - Arithmetic right-shift: R_{n-1} remains unchanged;
- R_{n-2} receives R_{n-1} , R_{n-3} receives R_{n-2} , so on.
- For a negative number, 1 is shifted from the sign bit to the right. A negative number is represented by the 2's complement. The sign bit remained unchanged.



Arithmetic Shift Right

- Arithmetic Shift Right :

- Example 1

0100 (4) \rightarrow 0010 (2)


- Example 2

1010 (-6) \rightarrow 1101 (-3)

Arithmetic Shift Left

The operation is same with Logic shift-left

 The only difference is you need to check overflow problem (Check **BEFORE** the shift)



Arithmetic Shift Left

- Arithmetic Shift Left :

- Example 1

0010 (2) \rightarrow 0100 (4)

- Example 2

1110 (-2) \rightarrow 1100 (-4)

Arithmetic Shift Left


- Arithmetic Shift Left :

- Example 3

0100 (4) \rightarrow 1000 (overflow)

- Example 4

1010 (-6) \rightarrow 0100 (overflow)

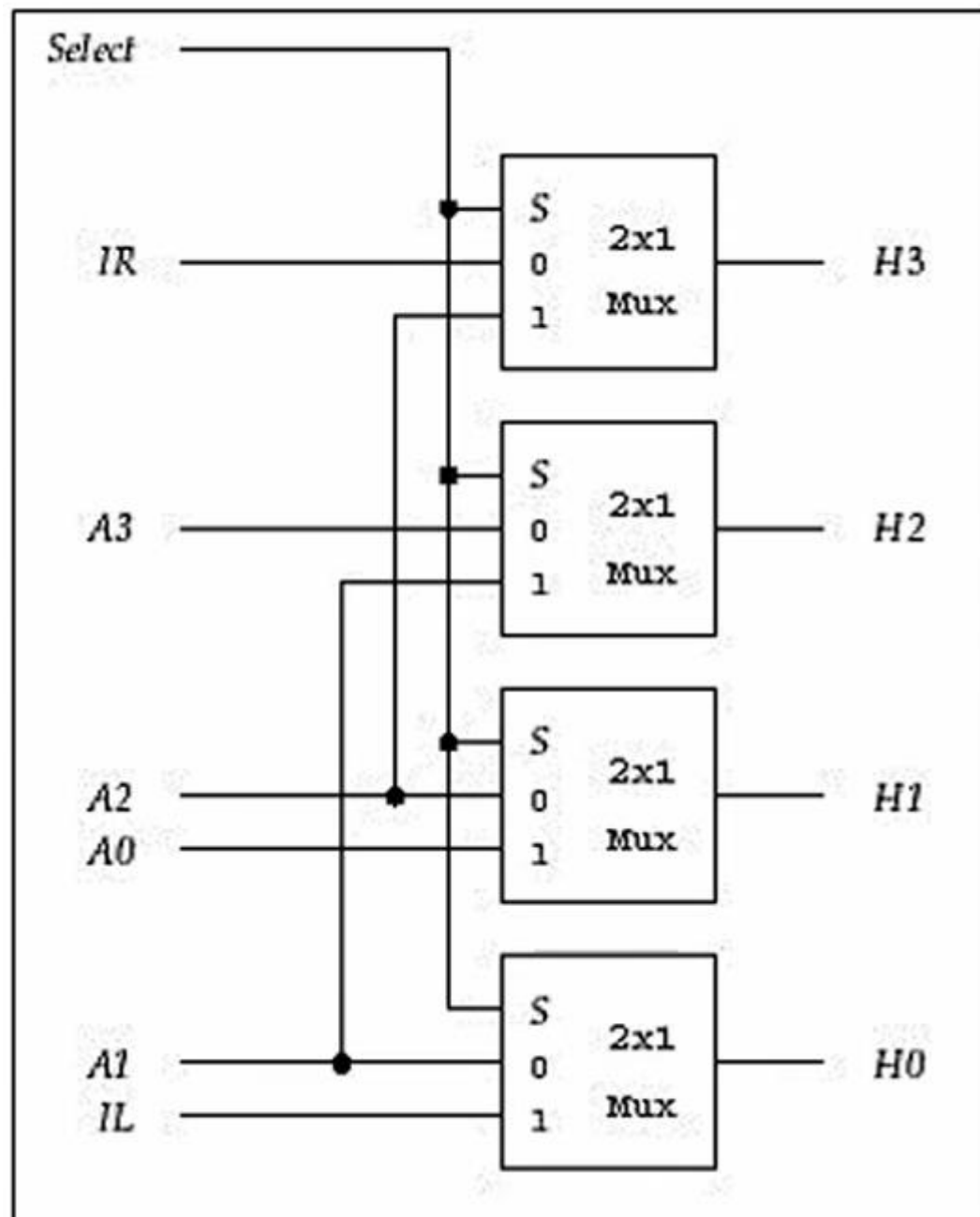

S	H ₃	H ₂	H ₁	H ₀
0	I _R	A ₃	A ₂	A ₁
1	A ₂	A ₁	A ₀	I _L

- S=0, shift right
- S=1, shift left

Error in the book

Example

- example: 011011

SHL 110110

SHR 001101

CL 110110


CLR 101101

ASHL Overflow

ASHR 001101

Arithmetic Logic Shift Unit

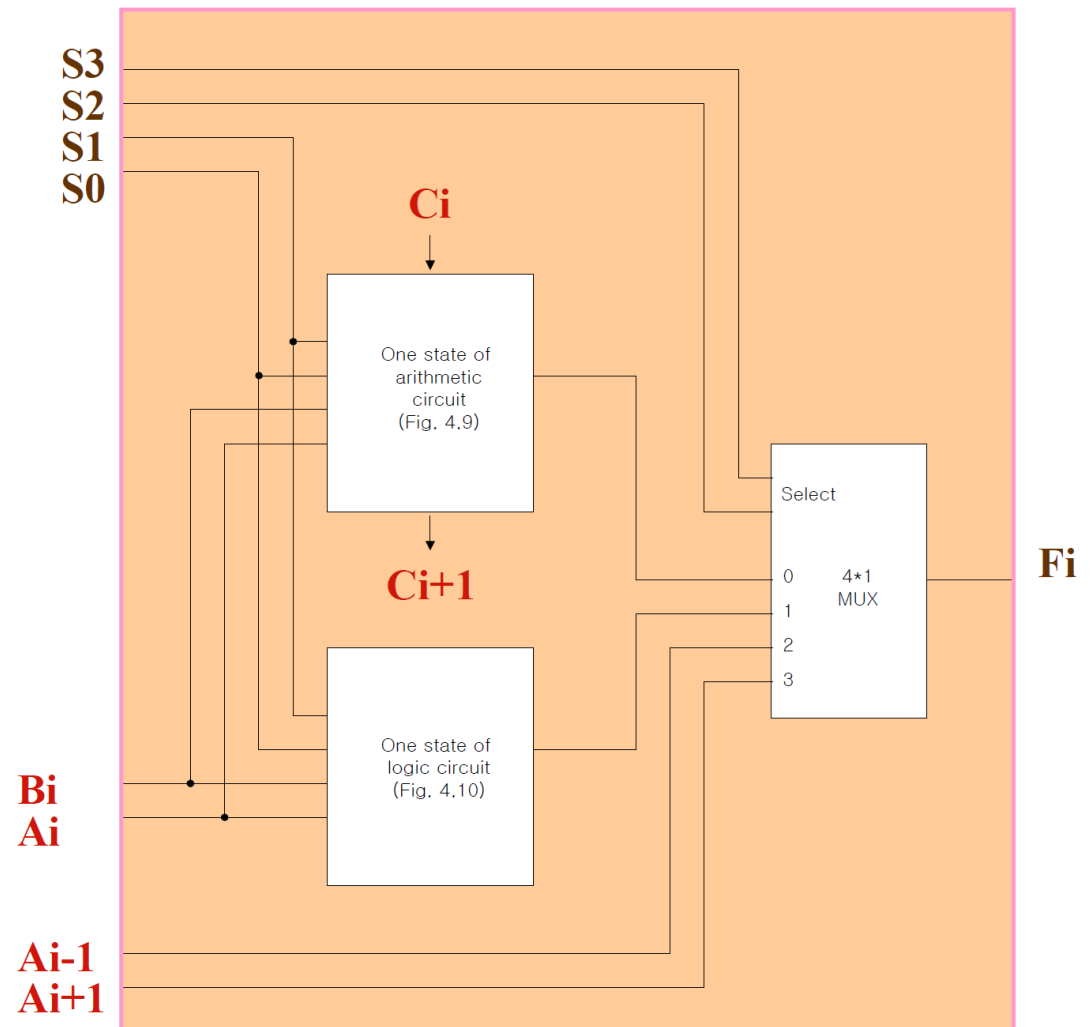One stage of arithmetic logic shift unit :



Operation select					Operation	Function
S_3	S_2	S_1	S_0	C_{in}		
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + \bar{B}$	Subtract with borrow
0	0	1	0	1	$F = A + \bar{B} + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	\times	$F = A \wedge B$	AND
0	1	0	1	\times	$F = A \vee B$	OR
0	1	1	0	\times	$F = A \oplus B$	XOR
0	1	1	1	\times	$F = \bar{A}$	Complement A
1	0	\times	\times	\times	$F = \text{shr } A$	Shift right A into F
1	1	\times	\times	\times	$F = \text{shl } A$	Shift left A into F