
Computer System Architecture

DR. Howida Youssry

Functions and Functional Blocks


- The functions considered are those found to be very useful in design
- Corresponding to each of the functions is a combinational circuit implementation called a *functional block*.

Binary Adder


★ Half Adder

- Adds **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

 
$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$



Binary Adder

★ Full Adder

 - Adds **1-bit** plus **1-bit** plus **1-bit**
- Produces **Sum** and **Carry**



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	y			
x	0	1	0	1
	1	0	1	0
		z		

$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

	y			
x	0	0	1	0
	0	1	1	1
		z		

$$C = xy + xz + yz$$



$$\begin{array}{r} x \\ + y \\ + z \\ \hline C \quad S \end{array}$$

Binary Adder

★ Full Adder



$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

 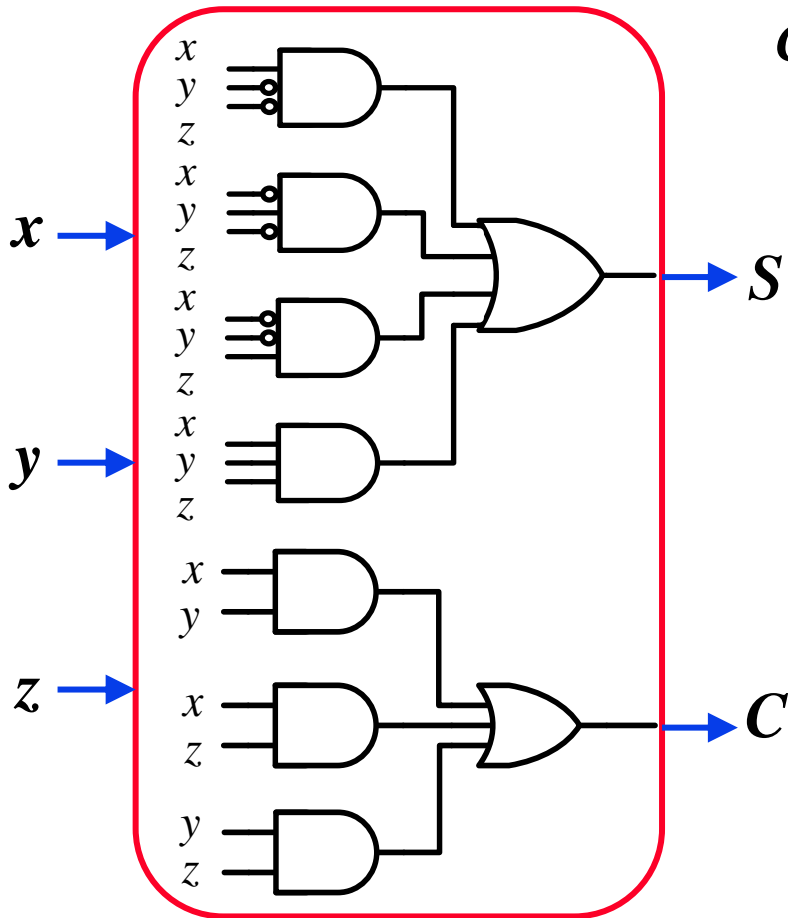


Binary Adder

★ Full Adder

  


Binary Adder

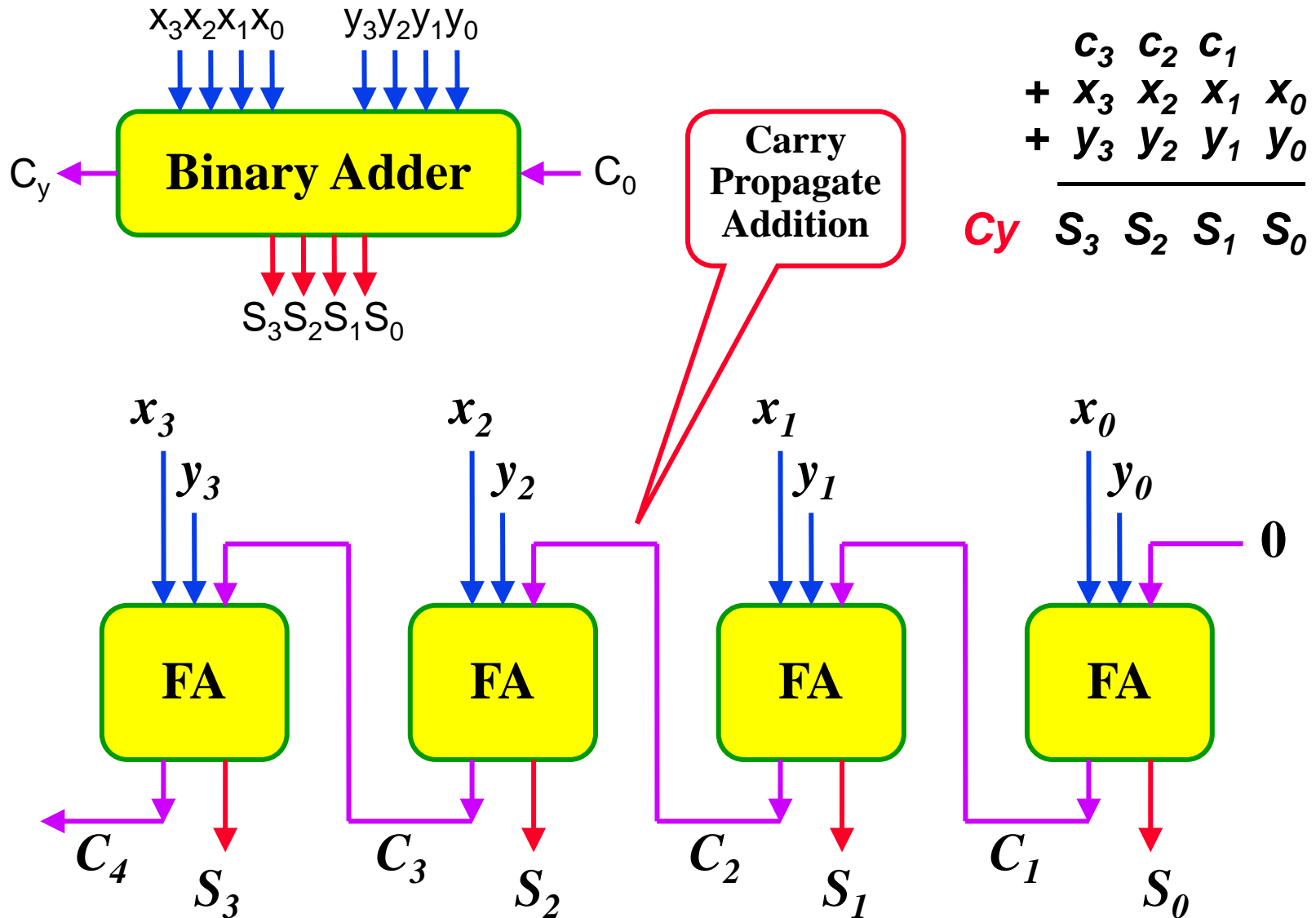

Binary Adder


★ Carry Propagate Adder

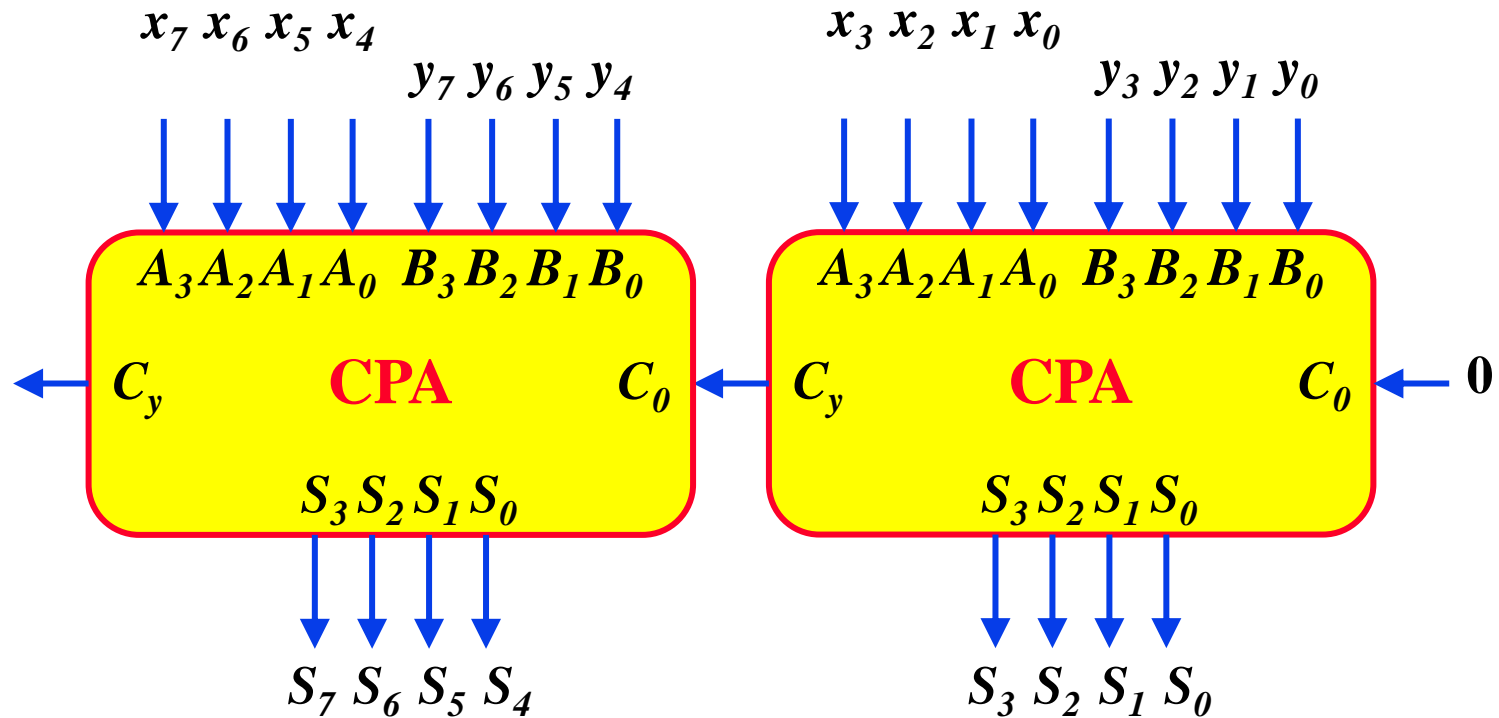


Selecting

- **Selecting of data or information is a critical function in digital systems and computers**
- **Circuits that perform selecting have:**
 - **A set of information inputs from which the selection is made**
 - **A single output**
 - **A set of control lines for making the selection**
- **Logic circuits that perform selecting are called *multiplexers***
- **Selecting can also be done by three-state logic or transmission gates**

Multiplexers


 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


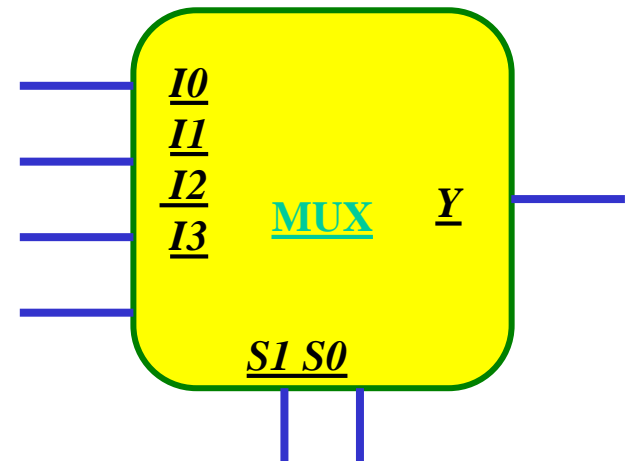


Multiplexers

■ 2-to-1 MUX

  




■ 4-to-1 MUX

 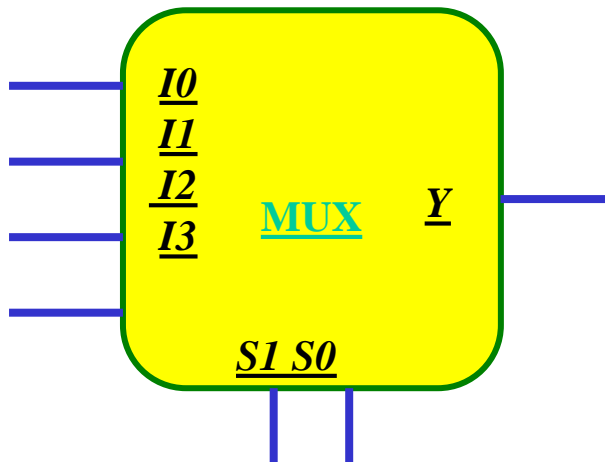

Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs

DeMultiplexers

   


S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

Multiplexer / DeMultiplexer

Pairs

MUX

DeMUX

 


Decoders

★ Extract “*Information*” from the code

★ Binary Decoder


- Example: 2-bit Binary Number

Only *one* lamp will turn on

 


Decoders

★ 2-to-4 Line Decoder

 

I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

$$Y_3 = I_1 I_0$$

$$Y_1 = \bar{I}_1 I_0$$

$$Y_2 = I_1 \bar{I}_0$$

$$Y_0 = \bar{I}_1 \bar{I}_0$$


Implementation Using Decoders

- ★ Each output is a minterm
- ★ All minterms are produced
- ★ Sum the required minterms

Example: Full Adder


$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

 


Implementation Using Decoders

Binary Decoder

 

Binary Decoder

 

Decoding


- Decoding - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called *decoders*
- Here, functional blocks for decoding are
 - called n -to- m line decoders, where $m \leq 2^n$, and
 - generate 2^n (or fewer) minterms for the n input variables

Encoders

★ Put “*Information*” into code

★ Binary Encoder

- Example: 4-to-2 Binary Encoder

 

Only *one* switch should be activated at a time

x_3	x_2	x_1	y_1	y_0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
1	0	0	1	1

Encoders



★ Octal-to-Binary Encoder (8-to-3)

I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$

$$Y_0 = I_7 + I_5 + I_3 + I_1$$

  


Encoding

- **Encoding - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code**
- **Circuits that perform encoding are called *encoders***
- **An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values**
- **Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.**

Encoder Example




- **A decimal-to-BCD encoder**
 - **Inputs:** 10 bits corresponding to decimal digits 0 through 9, (D_0, \dots, D_9)
 - **Outputs:** 4 bits with BCD codes
 - **Function:** If input bit D_i is a 1, then the output (A_3, A_2, A_1, A_0) is the BCD code for i ,
- **The truth table could be formed, but alternatively, the equations for each of the four outputs can be obtained directly.**

Encoder / Decoder Pairs

 

Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

   

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$

$$d = \dots$$



Combinational Function Implementation

★ Alternative implementation techniques:

- Decoders and OR gates
- Multiplexers (and inverter)
- ROMs
- PLAs
- PALs
- Lookup Tables

★ Can be referred to as *structured implementation methods* since a specific underlying structure is assumed in each case