 

Computer System Architecture

DR. Howida Youssry

REGISTER TRANSFER LANGUAGE

- A **digital system** is an interconnection of digital hardware **modules** that accomplish a specific information processing task.
- The various modules are *interconnected* with **common data** and **control paths** to form a digital computer system.



General Computer organization

Hardware Organization of Digital Computer


Hardware organization of a digital computer is defined by specifying:

- The **set of register** it contains and their function.
- The **sequence of micro-operations** performed on the binary information stored in the registers.
- The **control** that initiates the sequence of micro-operations

Digital Computer = Registers + Microoperations Hardware + Control Functions

MICROOPERATION

 An elementary operation performed during one clock pulse, on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

f: shift, count, clear, load, add,...

MICRO-OPERATIONS

Four types of microoperations

- **Register transfer microoperations**
- **Arithmetic microoperations**
- **Logic microoperations**
- **Shift microoperations**

REGISTER TRANSFER LANGUAGE (RTL)

- This is a **hardware description language** for digital system design.
- It allows you to specify the **data transfers and data manipulation** that can take place in a digital system.
- The **symbolic notation** used to describe the *microoperation* transfer among registers provides an organized and concise manner

Register Transfer


Basic Symbols for Register Transfers		
<u>Symbol</u>	<u>Description</u>	<u>Examples</u>
Letters & numerals	Denotes a register	MAR, R2
Parenthesis()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	$R2 \leftarrow R1$
Comma,	Separates two microoperations	$R2 \leftarrow R1, R1 \leftarrow R2$

Register Transfer (our first microoperation)


- Computer registers are designated by capital letters (sometimes followed by numerals) to denote the function of the register
 - R1: processor register
 - MAR: Memory Address Register (holds an address for a memory unit)
 - PC: Program Counter
 - IR: Instruction Register
 - SR: Status Register

Register Transfer (our first microoperation)

 - The individual flip-flops in an n-bit register are numbered in sequence from 0 to n-1 (from the right position toward the left position)



Register R1

 


Showing individual bits


A block diagram of a register

Register Transfer (our first microoperation)

 Other ways of drawing the block diagram of a register:




Numbering of bits

 


Partitioned into two parts

Register Notation

 


A simple register

 

Register showing bit positions



A Register showing individual bits

 

IR Register showing named portions
e.g. A(AD), A(Low), A(H),A(High)

Register Transfer (our first microoperation)

- Information transfer from one register to another is described by a replacement operator: **$R2 \leftarrow R1$**
- This statement denotes a transfer of the content of register R1 into register R2
- The transfer happens in one clock cycle
- The content of the R1 (source) does not change
- The content of the R2 (destination) will be lost and replaced by the new data transferred from R1

Register Transfer (our first microoperation)


- Conditional transfer occurs only under a control condition
- Representation of a (conditional) transfer
If ($P=1$) then $R2 \leftarrow R1$
- A binary condition (P equals to 0 or 1) determines when the transfer occurs
- The content of $R1$ is transferred into $R2$ only if P is 1

Register Transfer (our first microoperation)


Hardware implementation of a controlled transfer:

P: $R2 \leftarrow R1$

Block diagram:

 

Timing diagram

 

Register Transfer (our first microoperation)

Basic Symbols for Register Transfers		
<u><i>Symbol</i></u>	<u><i>Description</i></u>	<u><i>Examples</i></u>
Letters& numerals	Denotesaregister	MAR,R2
Parenthesis()	Denotesapartofa register	R2(0-7),R2(L)
Arrow←	Denotestransferof information	R2←R1
Comma,	Separatestwo microoperations	R2←R1,R1←R2


Bus and Memory Transfers

- Paths must be provided to transfer information from one register to another
- A Common Bus System is a scheme for transferring information between registers in a multiple-register configuration
- A bus: set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- Control signals determine which register is selected by the bus during each particular register transfer

Solution: Common Bus Solution

Common bus: is a set of common lines ,one for each bit of a register.

 
Control signals determine which register is the source, and which is the destination



$B \leftarrow A$
Dest \leftarrow Source

means that: $\text{Bus} \leftarrow \text{Source}$, then $\text{Dest} \leftarrow \text{Bus}$
 $\text{Bus} \leftarrow A$ $B \leftarrow \text{Bus}$

Bus and Memory Transfers

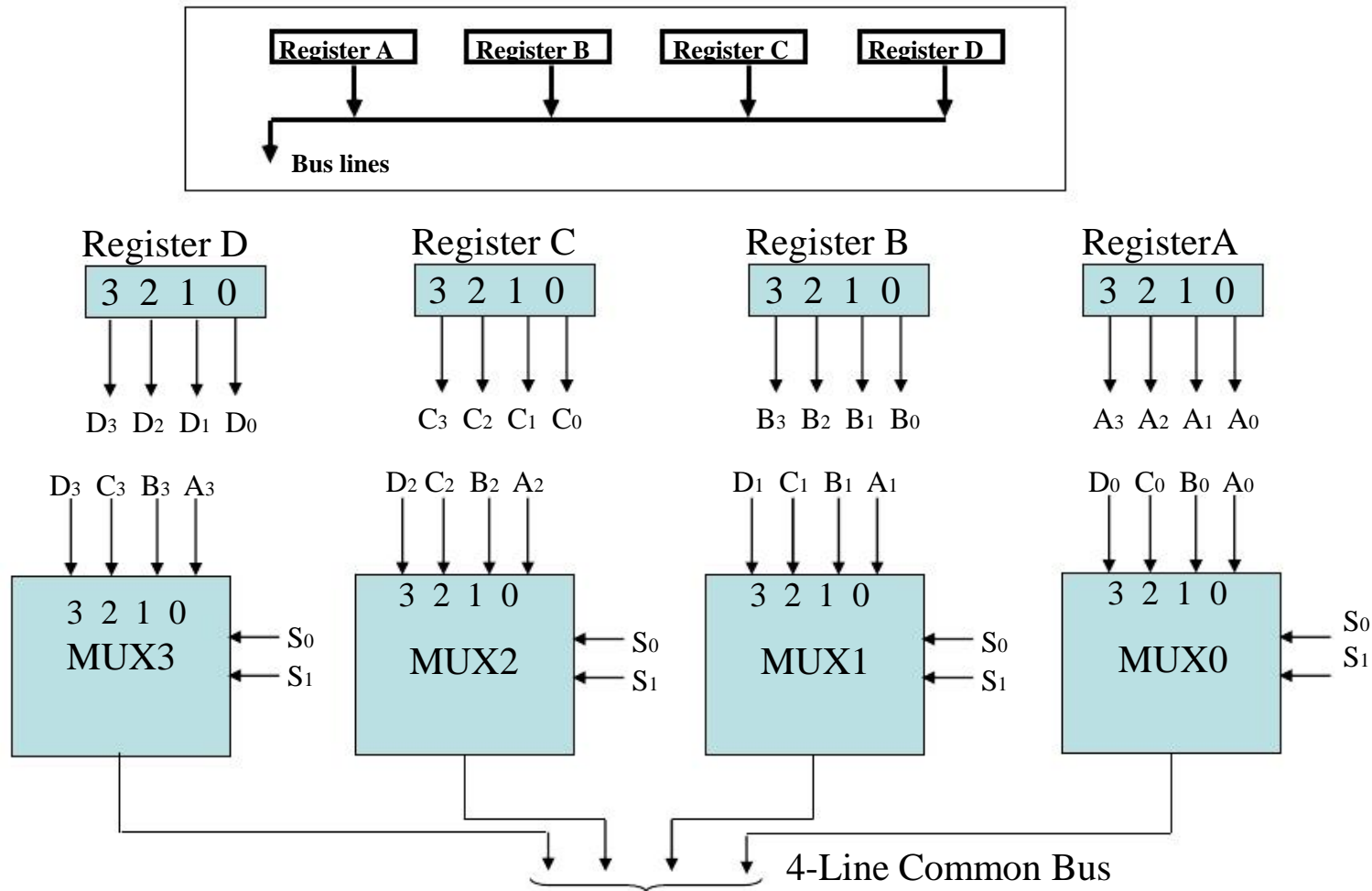

Bus and Memory Transfers

- Bus selection : two selection lines S1 and S0 are connected to the selection inputs of all four multiplexers.

S ₁	S ₀	Registerslected
0	0	A
0	1	B
1	0	C
1	1	D

Bus and Memory Transfers


- The transfer of information from a bus into one of many destination registers is done:
 - By connecting the bus lines to the inputs of all destination registers and then:
 - activating the load control of the particular destination register selected

$BUS \leftarrow C, R1 \leftarrow BUS$


- The content of register C is placed on the bus
- content of bus is loaded into register R1
- It is equivalent to: $R1 \leftarrow C$


Transfer from bus to a destination register.

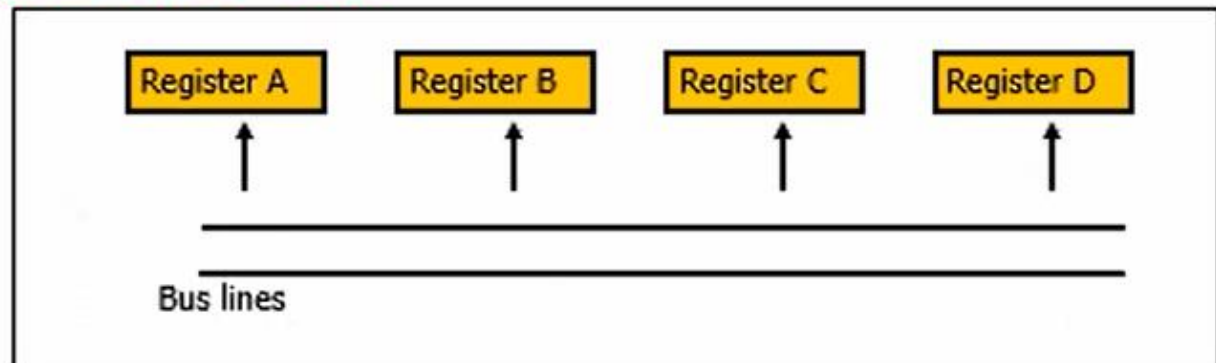From bus to register : $R \leftarrow bus$



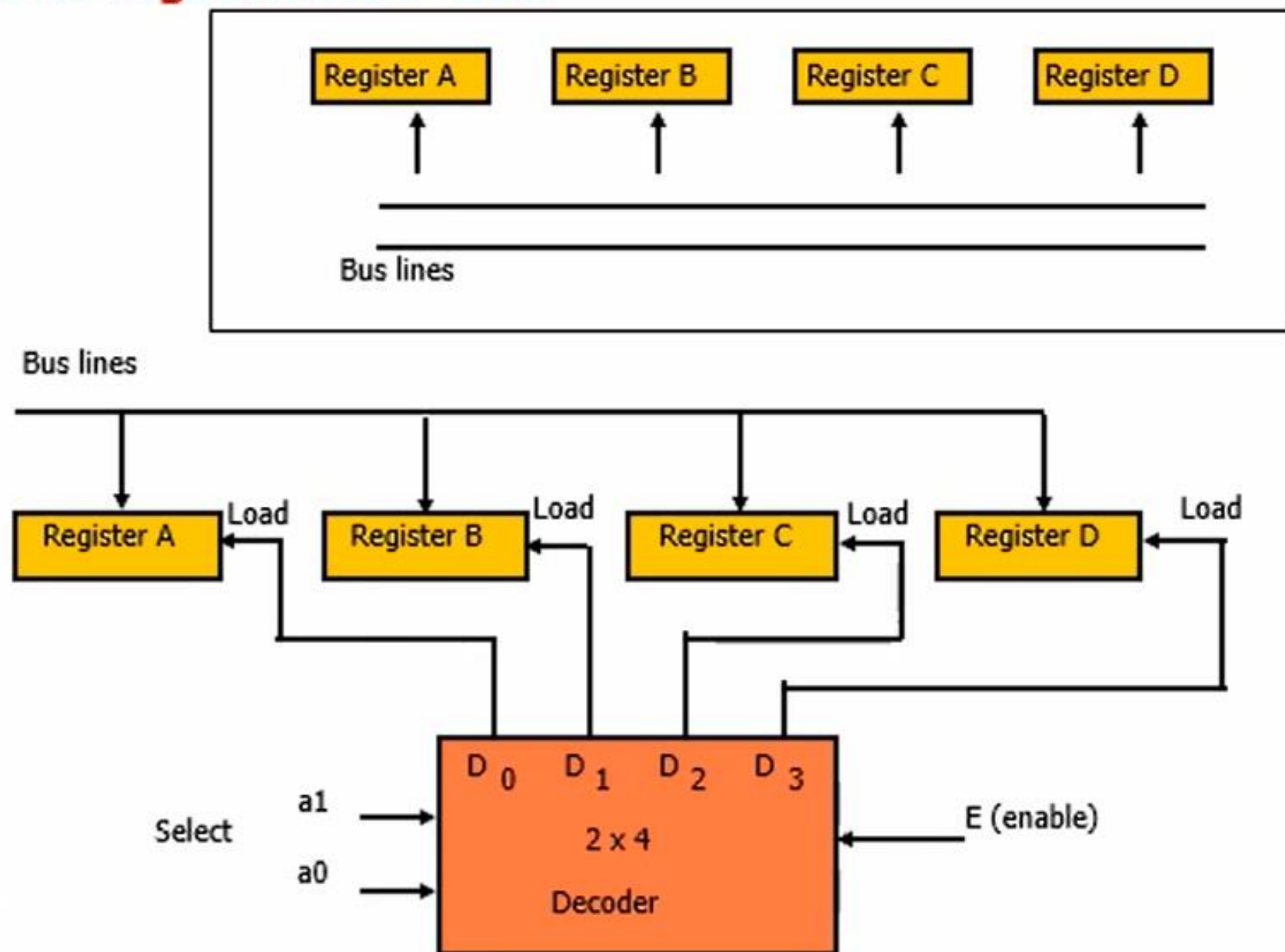From bus to register : $R \leftarrow \text{bus}$



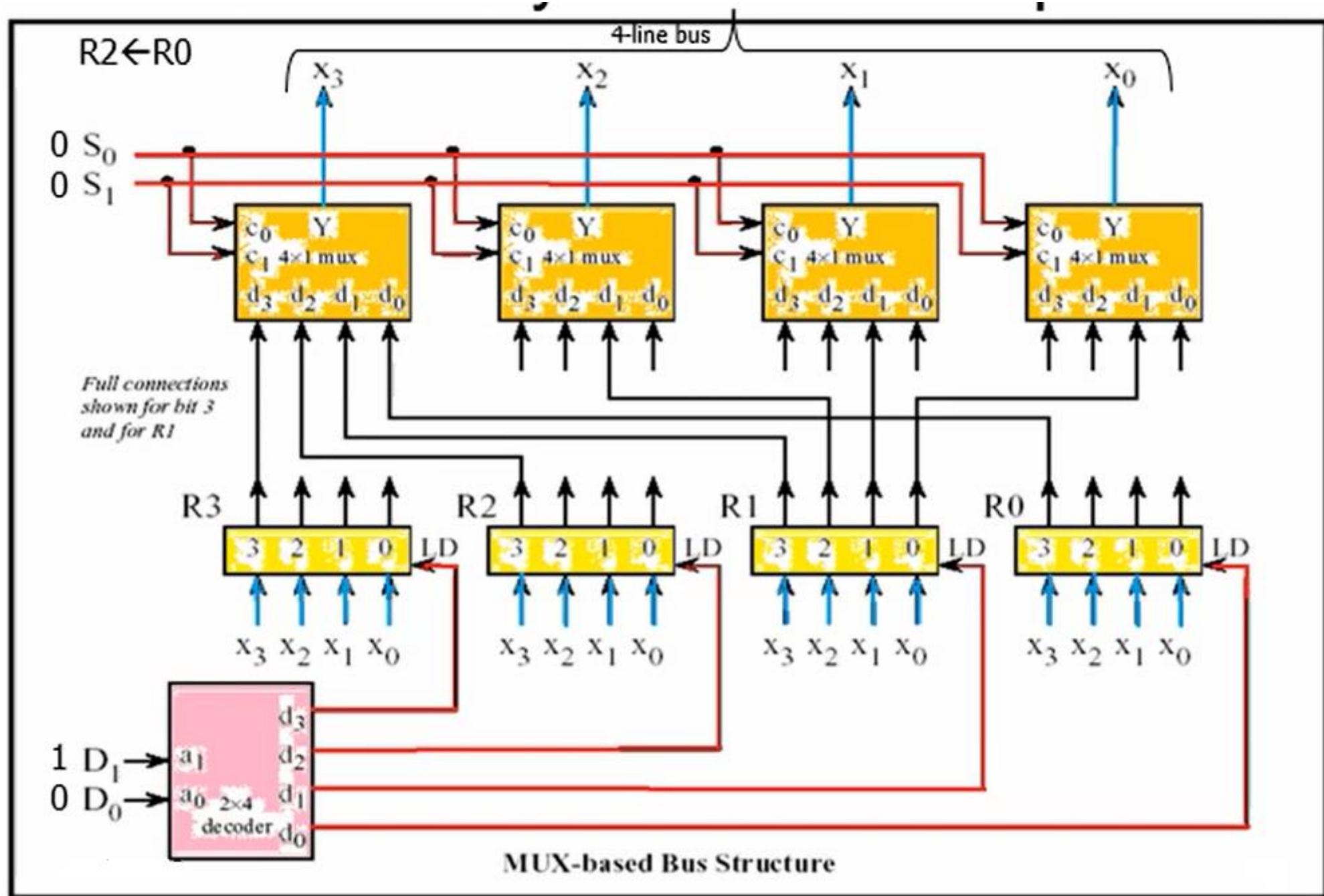


Memory Transfer

- ❑ **Read operation:** The transfer of information from a memory word to outside environment.

Read : $DR \leftarrow M[AR]$
(Bus $\leftarrow M[AR]$, $DR \leftarrow$ Bus)

- ❑ **Write operation:** The transfer of new information to be stored in memory.

 Write : $M[AR] \leftarrow R1$
(Bus $\leftarrow R1$, $M[AR] \leftarrow$ Bus)



Note:

AR: address register

DR: data register

4-3 Bus and Memory Transfers: Memory Transfer

- Memory read : Transfer from memory
- Memory write : Transfer to memory
- Data being read or wrote is called a memory word (called M)
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
- Example: M[0016] : the memory contents at address 0x0016

Bus and Memory Transfers: Memory Transfer

- Assume that the address of a memory unit is stored in a register called the Address Register AR
- Lets represent a Data Register with DR, then:
 - Read: $DR \leftarrow M[AR]$
 - Write: $M[AR] \leftarrow DR$

4-3 Bus and Memory Transfers: Memory Transfer

