
Computer System Architecture

DR. Howida Youssry

Digital Computers

Computer Hardware(H/W)

CPU

Memory

Program Memory(ROM)

Data Memory(RAM)

I/O Device

Input Device: Keyboard, Mouse,
Scanner

Output Device: Printer, Plotter,
Display

Storage Device(I/O): FDD, HDD,
MOD


 


Figure 1-1 Block Diagram of a digital Computer

Logic Gates

ADC(Analog to Digital Conversion)

 


Gate

The manipulation of binary information is done by logic circuit called “gate”.









Blocks of H/W that produce signals of binary 1 or 0 when input logic requirements are satisfied.

Digital Logic Gates : Fig. 1-2

 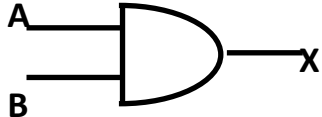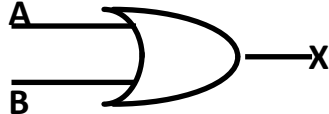AND, OR, INVERTER, BUFFER, NAND, NOR, XOR, XNOR



COMBINATIONAL GATES

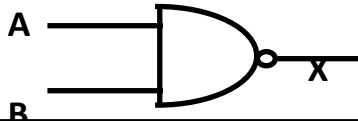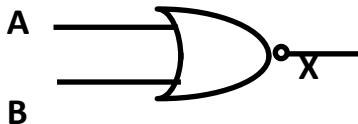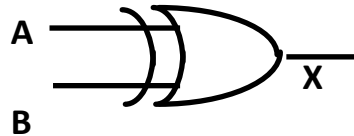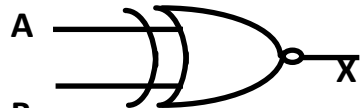Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND		$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR		$X = A \oplus B$ or $X = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR Exclusive NOR or Equivalence		$X = (A \oplus B)'$ or $X = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																


Boolean Algebra

Boolean Algebra

- * Algebra with Binary(Boolean) Variable and Logic Operations
- * Boolean Algebra is useful in Analysis and Synthesis of Digital Logic Circuits
 - Input and Output signals can be represented by Boolean Variables, and
 - Function of the Digital Logic Circuits can be represented by Logic Operations, i.e., Boolean Function(s)
 - From a Boolean function, a logic diagram can be constructed using AND, OR, and I

Truth Table

 - * The most elementary specification of the function of a Digital Logic Circuit is the Truth Table
 - Table that describes the Output Values for all the combinations of the Input Values, called *MINTERMS*
 - n input variables --> 2^n minterms



Boolean Algebra

Boolean Function: variable + operation

$$F(x, y, z) = x + y'z$$

Truth Table: *Fig. 1-3(a)*
Relationship between a function
and variable

**2^n Combination
Variable $n = 3$**


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Diagram: *Fig. 1-3(b)*

Algebraic Expression



Logic Diagram

 

Purpose of Boolean Algebra

To facilitate the analysis and design of digital circuit

Boolean function = **Algebraic form** = convenient tool

Truth table (relationship between binary variables : *Fig 1-3a*) \longrightarrow Algebraic form

Logic diagram (input-output relationship : *Fig. 1-3b*) \longrightarrow Algebraic form

Find simpler circuits for the same function : *by using Boolean algebra rules*

Boolean Algebra Rule : *Tab. 1-1*

[1] $x + 0 = x$	[2] $x \cdot 0 = 0$
[3] $x + 1 = 1$	[4] $x \cdot 1 = x$
[5] $x + x = x$	[6] $x \cdot x = x$
[7] $x + x' = 1$	[8] $x \cdot x' = 0$
[9] $x + y = y + x$	[10] $xy = yx$
[11] $x + (y + z) = (x + y) + z$	[12] $x(yz) = (xy)z$
[13] $x(y + z) = xy + xz$	[14] $x + yz = (x + y)(x + z)$
[15] $(x + y)' = x'y'$	[16] $(xy)' = x' + y'$
[17] $(x')' = x$	

[15] and [16] : De Morgan's Theorem

[ex.1]

$$\begin{aligned} F &= AB' + C'D + AB' + C'D \\ &= x + x \text{ (let } x = AB' + C'D) \\ &= x \\ &= AB' + C'D \end{aligned}$$

[ex.2]


$$\begin{aligned} F &= ABC + ABC' + A'C \\ &= AB(C + C') + A'C \\ &= AB + A'C \end{aligned}$$

Fig. 1-6(a)


Fig. 1-6(b)

1 inverter, 1 AND gate

Fig. 1-4 2 graphic symbols for NOR gate

 


(a) OR-invert

 


(b) invert-AND

Fig. 1-5 2 graphic symbols for NAND gate

 

(a) AND-invert

 

(b) invert-OR

EQUIVALENT CIRCUITS

Many different logic diagrams are possible for a given Function


$$F = ABC + ABC' + A'C \quad \text{.....} \quad (1)$$

$$= AB(C + C') + A'C \quad [13] \text{} \quad (2)$$


$$= AB \bullet 1 + A'C \quad [7]$$

$$= AB + A'C \quad [4] \text{} \quad (3)$$


(1)

 

(2)

 

(3)

 

COMPLEMENT OF FUNCTIONS

A Boolean function of a digital logic circuit is represented by only using logical variables and AND, OR, and Invert operators.

--> Complement of a Boolean function

- Replace all the variables and subexpressions in the parentheses appearing in the function expression with their respective complements

$$A, B, \dots, Z, a, b, \dots, z \Rightarrow A', B', \dots, Z', a', b', \dots, z'$$
$$(p + q) \Rightarrow (p + q)'$$

- Replace all the operators with their respective complementary operators


$$\text{AND} \Rightarrow \text{OR}$$
$$\text{OR} \Rightarrow \text{AND}$$

- Basically, extensive applications of the DeMorgan's theorem

$$(x_1 + x_2 + \dots + x_n)' \Rightarrow x_1' x_2' \dots x_n'$$

$$(x_1 x_2 \dots x_n)' \Rightarrow x_1' + x_2' + \dots + x_n'$$


SIMPLIFICATION

 

Simplification from Boolean function

- Finding an equivalent expression that is least expensive to implement
- For a simple function, it is possible to obtain a simple expression for low cost implementation
- But, with complex functions, it is a very difficult task

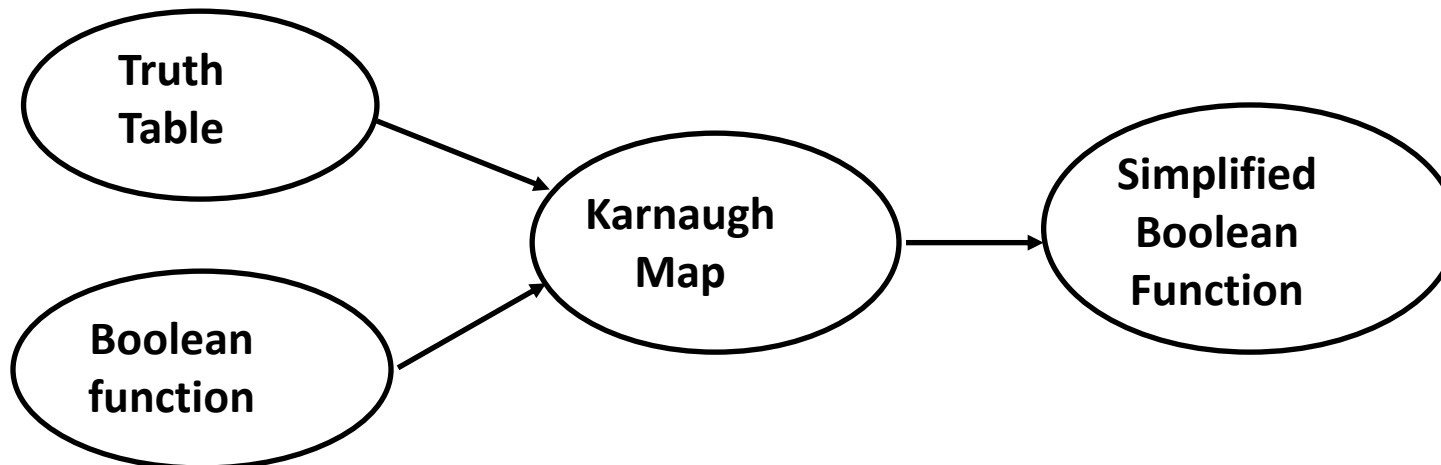Karnaugh Map(K-map) is a simple procedure for simplifying Boolean expressions.



Map Simplification

Karnaugh Map(K-Map)

Map method for simplifying Boolean expressions

Minterm / Maxterm

Minterm : n variables **product** ($x=1, x'=0$)

Maxterm : n variables **sum** ($x=0, x'=1$)

2 variables example

x	y	Minterm		Maxterm	
0	0	$x'y'$	m_0	$x + y$	M_0
0	1	$x'y$	m_1	$x + y'$	M_1
1	0	$x y'$	m_2	$x' + y$	M_2
1	1	$x y$	m_3	$x' + y'$	M_3

$$m_0 + m_1 + m_2 + m_3$$

$$M_0 \square M_1 \square M_2 \square M_3$$

$$F = \underbrace{x'y}_{m_1} + \underbrace{xy}_{m_3}$$

$$= \odot(1,3) \quad (m_1 + m_3)$$

$$= \angle(0,2) \quad (\text{Complement} = M_0 \square M_2)$$

KARNAUGH MAP

Karnaugh Map for an n-input digital logic circuit (n-variable sum-of-products form of Boolean Function, or Truth Table) is

- Rectangle divided into 2^n cells
 - Each cell is associated with a *Minterm*
 - An output(function) value for each input value associated with a minterm is written in the cell representing the minterm
- > 1-cell, 0-cell

Each Minterm is identified by a decimal number whose binary representation is identical to the binary interpretation of the input values of the minterm.

x	F
0	1
1	0

x	
0	0
1	1

Identification of the cell

Karnaugh Map

x	
0	0
1	1

value of F

$$F(x) = \sum (1)$$

1-cell

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

	y	0	1
x	0	0	1
	1	1	1

	y	0	1
x	0	0	1
	1	1	0

$$F(x,y) = \sum (1,2)$$

KARNAUGH MAP

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

		y			
		00	01	11	10
x\yz	0	0	1	3	2
	1	4	5	7	6

		yz			
		00	01	11	10
x	0	0	1	0	1
	1	1	0	0	0

$$F(x,y,z) = \sum (1,2,4)$$

u	v	w	x	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

		w			
		00	01	11	10
uv\wx	00	0	1	3	2
	01	4	5	7	6
u	11	12	13	15	14
	10	8	9	11	10

		wx			
		00	01	11	10
uv	00	0	1	1	0
	01	0	0	0	1
u	11	0	0	0	1
	10	1	1	1	0

$$F(u,v,w,x) = \sum (1,3,6,8,9,11,14)$$


Ex) $F = x + y'z$

(1) Truth Table

x	y	z	F	Minterm
0	0	0	0	m ₀
0	0	1	1	m ₁
0	1	0	0	m ₂
0	1	1	0	m ₃
1	0	0	1	m ₄
1	0	1	1	m ₅
1	1	0	1	m ₆
1	1	1	1	m ₇

(2) $F(x, y, z) = \sum(1, 4, 5, 6, 7)$

(3)

 

[ex.] $F(A,B,C) = \Sigma(3,4,6,7)$

$$F = AC' + BC$$

[ex.] $F(A,B,C) = \Sigma(0,2,4,5,6)$

$$F = C' + AB'$$

[ex.] $F(A,B,C,D) = \Sigma(0,1,2,6,8,9,10)$

$$F = B'D' + B'C' + A'CD'$$

Product-of-Sums Simplification

$$F(A,B,C,D) = \Sigma(0,1,2,5,8,9,10)$$

$$F = B'D' + B'C' + A'C'D$$


Sum of product

$$F' = AB + CD + BD' \text{ (square marked 0's)}$$

$$F''(F) = (A' + B')(C' + D')(B' + D)$$

전개


Product of Sum

 

Combinational Circuits

A connected arrangement of *logic gates* with a set of inputs and outputs


Fig. 1-15 Block diagram of a combinational circuit

 

A sequential circuit

is an interconnection of F/F and Gate

Clocked synchronous sequential circuit

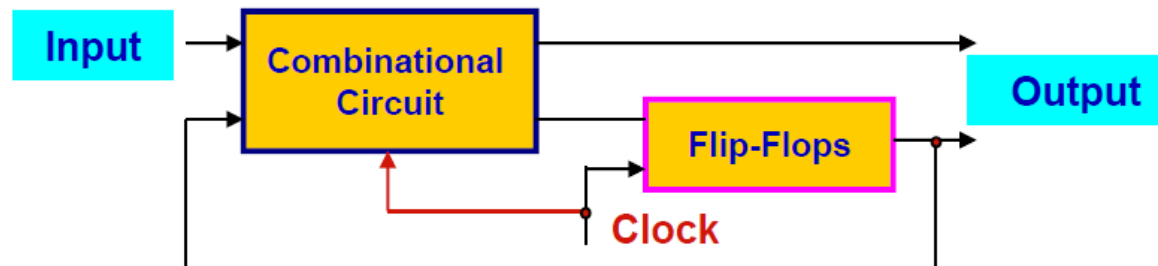

Flip-Flops


Flip-Flop

Combinational Circuit = Gate
Sequential Circuit = Gate + F/F

The *storage elements* employed in clocked *sequential circuit*


A binary cell capable of storing one bit of information

SR(*Set/Reset*) F/F

 

S	R	Q(t+1)
0	0	Q(t) no change
0	1	0 clear to 0
1	0	1 set to 1
1	1	? Indeterminate

D(*Data*) F/F

 


D	Q(t+1)
0	0 clear to 0
1	1 set to 1

“no change” condition : $Q(t+1)=D$


- 1) Disable Clock
- 2) Feedback output into input p.52

JK(*Jack/King*) F/F

 

J	K	Q(t+1)
0	0	Q(t) no change
0	1	0 clear to 0
1	0	1 set to 1
1	1	Q(t)' Complement

T(*Toggle*) F/F

 

T	Q(t+1)
0	Q(t) no change
1	Q'(t) Complement


JK F/F is a refinement of the SR F/F
The indeterminate condition of the SR type is defined in complement

$T=1(J=K=1)$, $T=0(J=K=0)$ 이면 JK F/F
수식 표현 : $Q(t+1) = Q(t) \oplus T$ xor

1-7 Sequential Circuits

A sequential circuit is an interconnection of F/F and Gate

Clocked synchronous sequential circuit

 

Combinational Circuit = Gate
Sequential Circuit = Gate + F/F

Input Equation

$$D_A = AX + BX, D_B = A'x$$

Output Equation

$$y = Ax' + Bx'$$

Fig. 1-25 Example of a sequential circuit

