

---


# Computer System Architecture

DR. Howida Youssry

---


# MEMORY COMPONENTS

## Logical Organization

 

 
## Random Access Memory

- Each word has a unique address
- Access to a word requires the same time independent of the location of the word
- Organization



# Memory Components

 


Select = 0 (cell disable)  
Select = 1 (cell enable)


Memory address		Memory contents
Binary	Decimal	
0000000000	0	10110101 01011100
0000000001	1	10101011 10001001
0000000010	2	00001101 01000110
	⋮	⋮
	⋮	⋮
	⋮	⋮
	⋮	⋮
1111111101	1021	10011101 00010101
1111111110	1022	00001101 00011110
1111111111	1023	11011110 00100100

Contents of a  $1024 \times 16$  Memory

# Memory Components

 


(a) Logic diagram

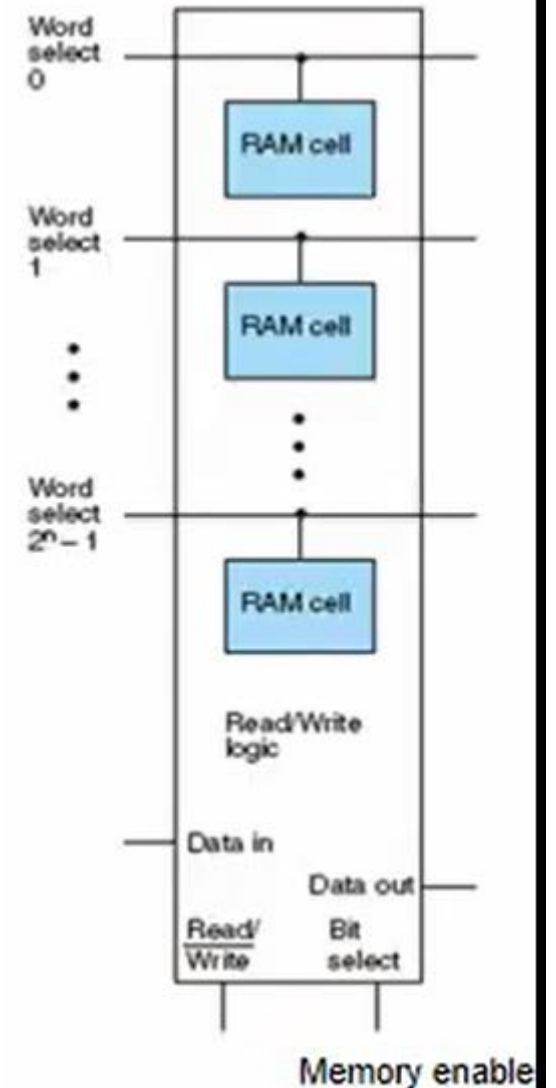

Control Inputs to Memory Chip


Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

# Memory Components

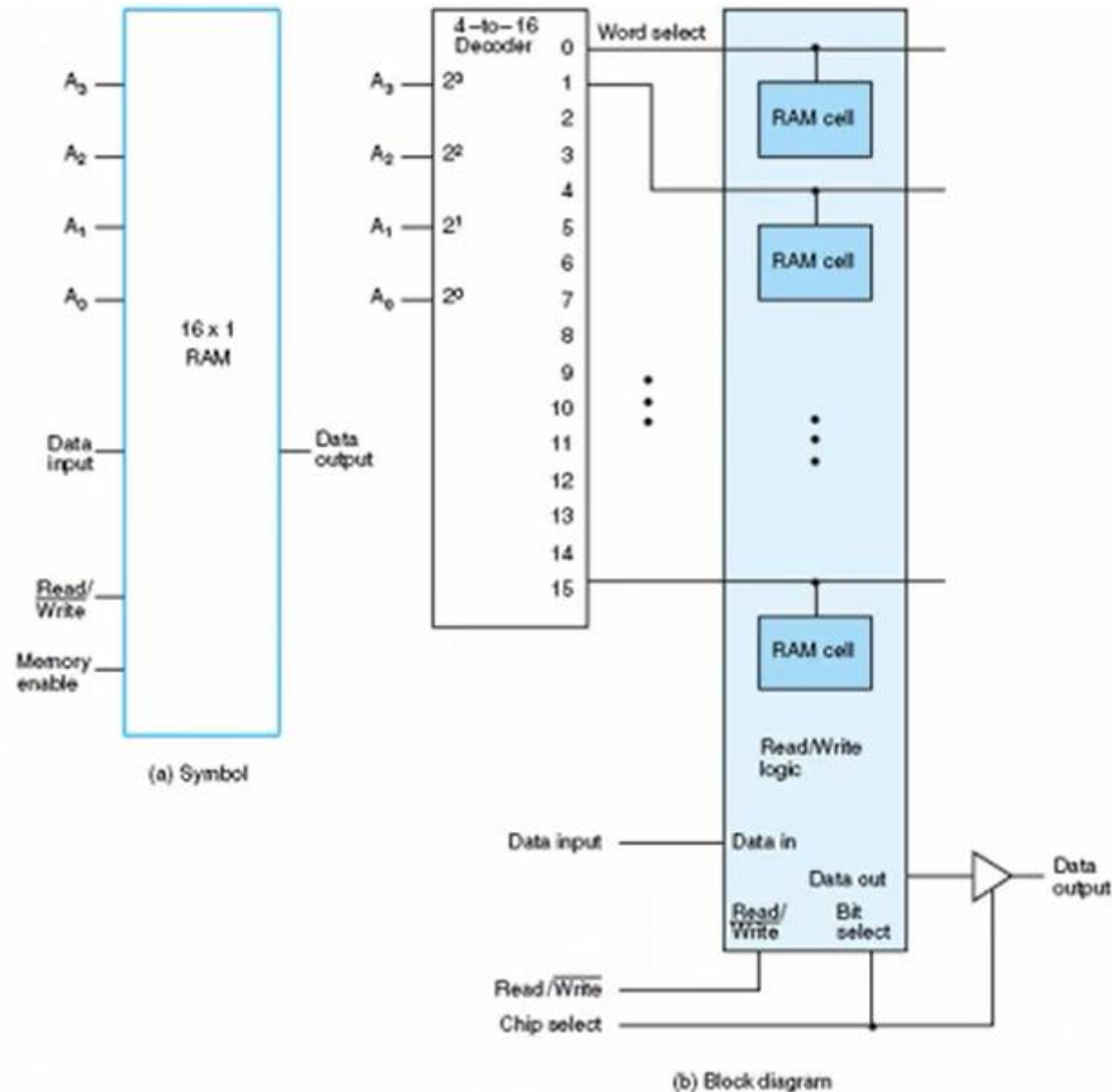

16-Word by 1-Bit RAM Chip

# Memory Components

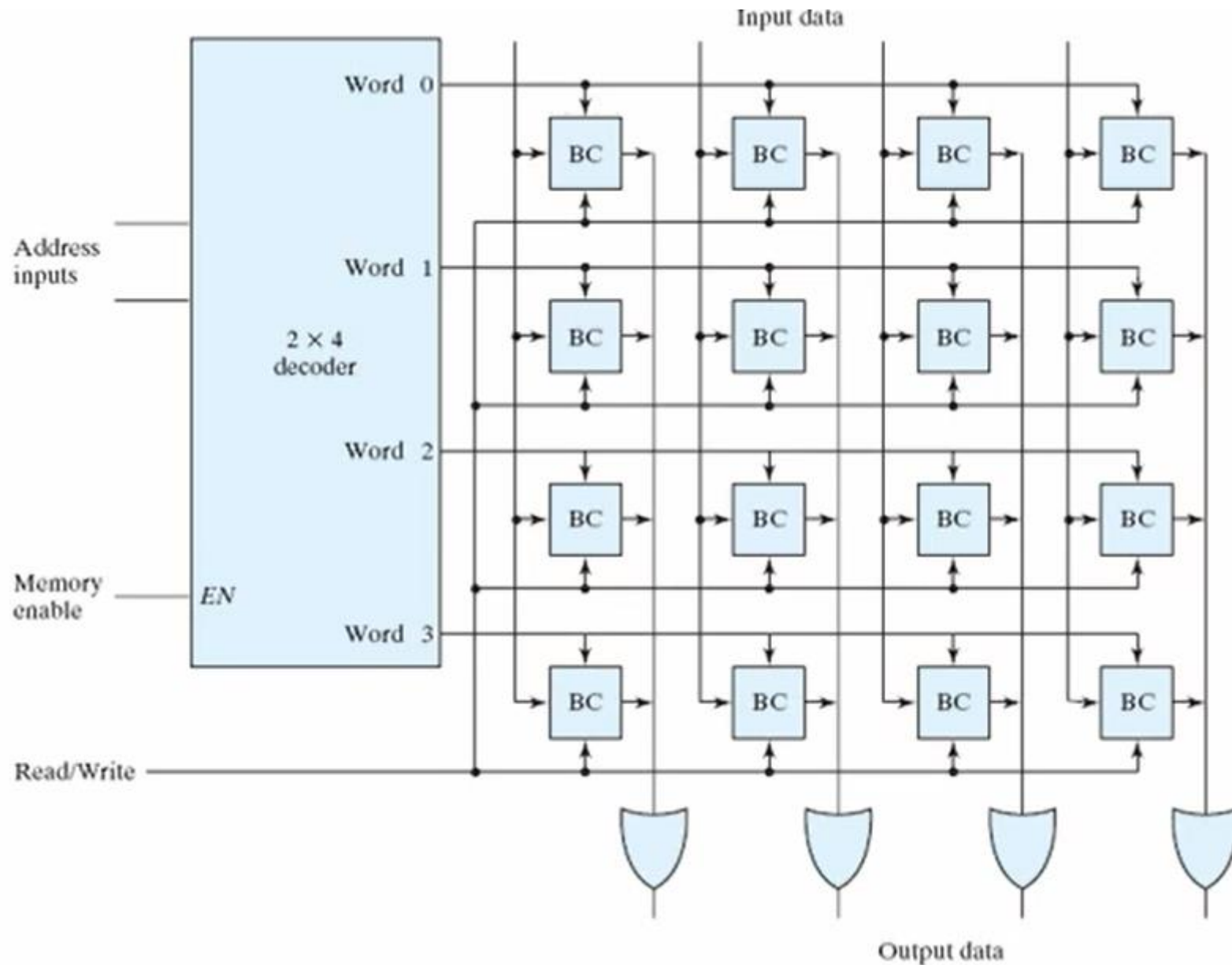

# READ ONLY MEMORY(ROM)

## Characteristics

- Perform read operation only, write operation is not possible
- Information stored in a ROM is made permanent during production, and cannot be changed
- Organization

k address input lines



n data output lines

Information on the data output line depends only on the information on the address input lines.

--> Combinational Logic Circuit

$$\begin{aligned} X_0 &= A'B' + B'C \\ X_1 &= A'B'C + A'BC' \\ X_2 &= BC + AB'C' \\ X_3 &= A'BC' + AB' \\ X_4 &= AB \end{aligned}$$

$$\begin{aligned} X_0 &= A'B'C' + A'B'C + AB'C \\ X_1 &= A'B'C + A'BC' \\ X_2 &= A'BC + AB'C' + ABC \\ X_3 &= A'BC' + AB'C' + AB'C \\ X_4 &= ABC' + ABC \end{aligned}$$


Canonical minterms

address


Output

ABC	$X_0$	$X_1$	$X_2$	$X_3$	$X_4$
000	1	0	0	0	0
001	1	1	0	0	0
010	0	1	0	1	0
011	0	0	1	0	0
100	0	0	1	1	0
101	1	0	0	1	0
110	0	0	0	0	1
111	0	0	1	0	1

# READ ONLY MEMORY(ROM)

 

Internal Logic of a  $32 \times 8$  ROM

 

Block Diagram of ROM



# **TYPES OF ROM**

## **ROM**

- **Store information (function) during production**
- **Mask is used in the production process**
- **Unalterable**
- **Low cost for large quantity production --> used in the final products**

## **PROM (Programmable ROM)**

- **Store info electrically using PROM programmer at the user's site**
- **Unalterable**
- **Higher cost than ROM -> used in the system development phase**
  - > **Can be used in small quantity system**

## **EPROM (Erasable PROM)**

- **Store info electrically using PROM programmer at the user's site**
- **Stored info is erasable (alterable) using UV light (electrically in some devices) and rewriteable**
- **Higher cost than PROM but reusable --> used in the system development phase. Not used in the system production due to erasability**

# **INTEGRATED CIRCUITS**

## **Classification by the Circuit Density**


- SSI - several (less than 10) independent gates**
- MSI - 10 to 200 gates; Perform elementary digital functions;  
Decoder, adder, register, parity checker, etc**
- LSI - 200 to few thousand gates; Digital subsystem  
Processor, memory, etc**
- VLSI - Thousands of gates; Digital system  
Microprocessor, memory module**

## **Classification by Technology**

- TTL - Transistor-Transistor Logic  
Bipolar transistors  
NAND**
- ECL - Emitter-coupled Logic  
Bipolar transistor  
NOR**
- MOS - Metal-Oxide Semiconductor  
Unipolar transistor  
High density**
- CMOS - Complementary MOS  
Low power consumption**
 
# REGISTER TRANSFER LANGUAGE

- A **digital system** is an interconnection of digital hardware **modules** that accomplish a specific information processing task.
- The various modules are *interconnected* with **common data** and **control paths** to form a digital compute system.



General Computer organization

# Hardware Organization of Digital Computer

Hardware organization of a digital computer is defined by specifying:

- The **set of register** it contains and their function.
- The **sequence of micro-operations** performed on the binary information stored in the registers.
- The **control** that initiates the sequence of micro-operations

# Micro-operation

Micro-operations are the basis for microprocessors.

The operation executed on data stored in register are called **micro-operation**


That is, a microprocessor performs the micro-operations in order to realize *the instruction*.

- An instruction is fetched from memory, decoded and executed by performing a sequence of micro-operations.

The micro-operations only specify which data transfers may occur; they don't specify when or how they may occur.
 
# MICROOPERATION

An elementary operation performed during one clock pulse, on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

f: shift, count, clear, load, add,...

# MICRO-OPERATIONS

## Four types of microoperations

- Register transfer microoperations
- Arithmetic microoperations
- Logic microoperations
- Shift microoperations

## \* Summary of Arithmetic Micro-Operations

$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

# REGISTER TRANSFER LANGUAGE

**For any function of the computer, a sequence of microoperations is used to describe it**

**----> *Register transfer language***

- A symbolic language**
- A convenient tool for describing the internal organization of digital computers**
- Can also be used to facilitate the design process of digital systems.**




# REGISTER TRANSFER

**Designation of a register**

- a register
- portion of a register
- a bit of a register

**Common ways of drawing the block diagram of a register**

Register

 


15

0



Numbering of bits


Showing individual bits

 

15

8 7

0

 

Subfields

**Representation of a transfer(parallel)**

$R2 \leftarrow R1$

A simultaneous transfer of all bits from the source to the destination register, during one clock pulse

**Representation of a controlled(conditional) transfer**

P:  $R2 \leftarrow R1$


A binary condition( $p=1$ ) which determines when the transfer is to occur

If ( $p=1$ ) then ( $R2 \leftarrow R1$ )


HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS

Implementation of controlled transfer  
P:  $R2 \leftarrow R1$

Block diagram

 

Timing diagram

 

Basic Symbols for Register Transfers

Symbols	Description	Meaning
Capital letters and numerals	Denotes a register	MAR, R2
Parentheses ( )	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	$A \leftarrow B, B \leftarrow A$

