

Latches & Flip-flops

Sequential Logic

Latches & Flip-flops

- Introduction
- Memory Elements
- Pulse-Triggered Latch
 - ❖ S-R Latch
 - ❖ Gated S-R Latch
 - ❖ Gated D Latch
- Edge-Triggered Flip-flops
 - ❖ S-R Flip-flop
 - ❖ D Flip-flop
 - ❖ J-K Flip-flop
 - ❖ T Flip-flop
- Asynchronous Inputs

Flip-Flops & Latches

- Review sequential logic and the flip-flop.
- Introduce the D flip-flop and provide an excitation table and a sample timing analysis.
- Introduce the J/K flip-flop and provide an excitation table and a sample timing analysis.
- Review flip-flop clock parameters.
- Introduce the transparent D-latch.
- Discuss flip-flop asynchronous inputs.

Flip-Flops & Latches


- Sequential switching network
 - Output depends on present input and past sequence of inputs.
 - Need to remember past history.
 - Flip-flop (latch) is a memory that has a pair of complementary outputs.

Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information

Introduction

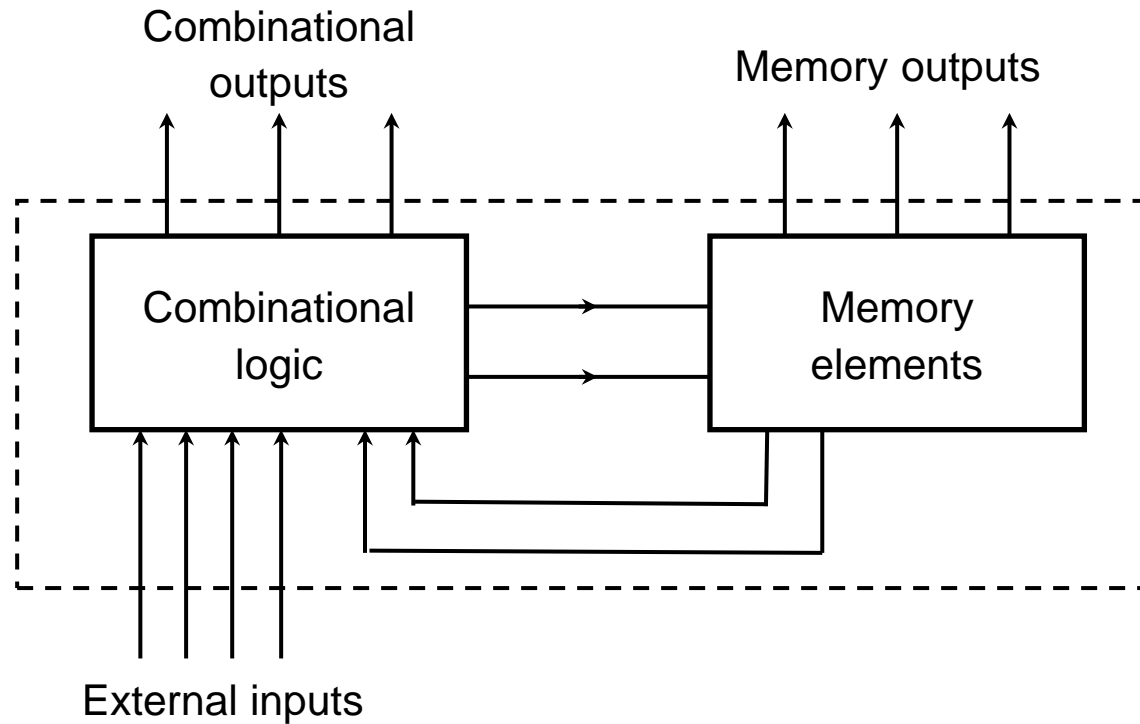- A **sequential circuit** consists of a *feedback path*, and employs some *memory elements*.



Sequential circuit = Combinational logic + Memory Elements

Introduction


- There are two types of sequential circuits:
 - ❖ *synchronous*: outputs change only at specific time
 - ❖ *asynchronous*: outputs change at any time
- *Multivibrator*: a class of sequential circuits. They can be:
 - ❖ *bistable* (2 stable states)
 - ❖ *monostable* or *one-shot* (1 stable state)
 - ❖ *astable* (no stable state)
- Bistable logic devices: *latches* and *flip-flops*.
- Latches and flip-flops differ in the method used for changing their state.

Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has *memory*.
- Some definitions:
 - **State:** all the information about a circuit necessary to explain its future behavior
 - **Latches and flip-flops:** state elements that store one bit of state
 - **Synchronous sequential circuits:** combinational logic followed by a bank of flip-flops

Memory Elements

 - **Memory element**: a device which can remember value indefinitely, or change value on command from its inputs.




- **Characteristic table**:

| Command (at time t) | $Q(t)$ | $Q(t+1)$ |
|---------------------------|--------|----------|
| Set | X | 1 |
| Reset | X | 0 |
| Memorise / No Change | 0 | 0 |
| | 1 | 1 |


$Q(t)$: current state
 $Q(t+1)$ or Q^+ : next state

Memory Elements

 - Memory element with clock. Flip-flops are memory elements that change state on clock signals.



- Clock is usually a square wave.

 

Memory Elements



- Two types of triggering/activation:
 - ❖ pulse-triggered
 - ❖ edge-triggered
- Pulse-triggered
 - ❖ latches
 - ❖ ON = 1, OFF = 0
- Edge-triggered
 - ❖ flip-flops
 - ❖ positive edge-triggered (ON = from 0 to 1; OFF = other time)
 - ❖ negative edge-triggered (ON = from 1 to 0; OFF = other time)

State Elements

- The state of a circuit influences its future behavior
- State elements store state
 - Bistable circuit
 - SR Latch
 - D Latch
 - D Flip-flop



Bistable Circuit

  - Fundamental building block of other state elements
- Two outputs: Q , \overline{Q}
- No inputs



Bistable Circuit Analysis

  - Consider the two possible cases:
 - $Q = 0$:
then $Q = 1$, $\bar{Q} = 0$ (consistent)
 - $Q = 1$:
then $Q = 0$, $\bar{Q} = 1$ (consistent)
- Stores 1 bit of state in the state variable, Q (or \bar{Q})
- But there are **no inputs to control the state**




S-R Latch

- *Complementary* outputs: Q and Q' .
- When Q is HIGH, the latch is in *SET* state.
- When Q is LOW, the latch is in *RESET* state.
- For *active-HIGH input S-R latch* (also known as NOR gate latch),
 - R =HIGH (and S =LOW) a RESET state
 - S =HIGH (and R =LOW) a SET state
 - both inputs LOW a no change
 - both inputs HIGH a Q and Q' both LOW (invalid)!

S-R Latch


- Characteristics table for active-high input S-R latch:

| <i>S</i> | <i>R</i> | <i>Q</i> | <i>Q'</i> | |
|----------|----------|----------|-----------|---|
| 0 | 0 | NC | NC | No change. Latch remained in present state. |
| 1 | 0 | 1 | 0 | Latch SET. |
| 0 | 1 | 0 | 1 | Latch RESET. |
| 1 | 1 | 0 | 0 | Invalid condition. |

 


S-R Latch

■ Active-HIGH input S-R latch

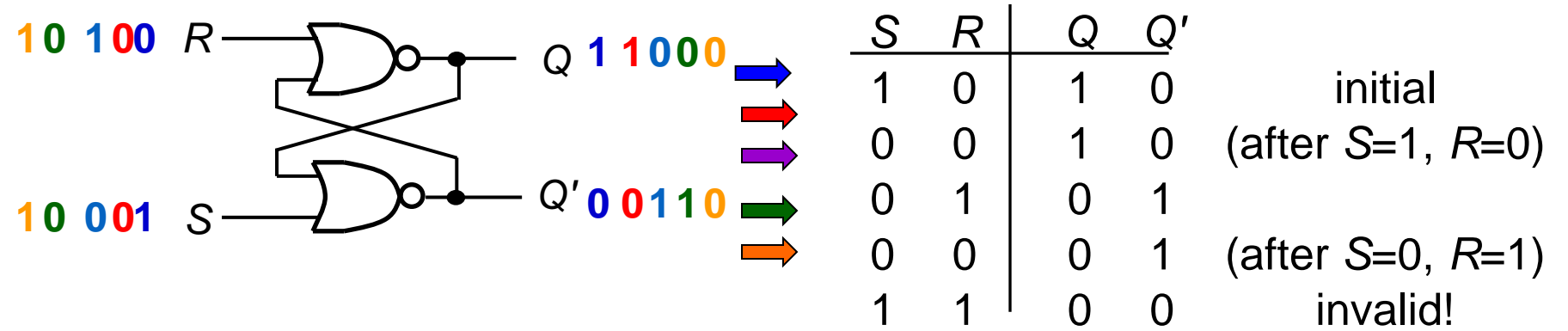

SR (Set/Reset) Latch

- SR Latch

 


- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$

SR Latch Analysis


– $S = 1, R = 0$:

then $Q = 1$ and $\overline{Q} = 0$

 

– $S = 0, R = 1$:



then $\overline{Q} = 1$ and $Q = 0$

 

SR Latch Analysis


– $S = 0, R = 0$:

then $Q = Q_{prev}$

  

– $S = 1, R = 1$:

then $Q = 0, \bar{Q} = 0$


 


SR Latch Analysis

– $S = 0, R = 0$:

then $Q = Q_{prev}$

– **Memory!**

  


– $S = 1, R = 1$:

then $Q = 0, \overline{Q} = 0$

– **Invalid State**


$\overline{Q} \neq \text{NOT } Q$

 

SR Latch Symbol



- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S , R inputs
 - **Set:** Make the output 1
($S = 1$, $R = 0$, $Q = 1$)
 - **Reset:** Make the output 0
($S = 0$, $R = 1$, $Q = 0$)
- **Must do something to avoid invalid state (when $S = R = 1$)**

SR Latch
Symbol

 

Gated D Latch

  - Make R input equal to S' \rightarrow *gated D latch*.
- D latch eliminates the undesirable condition of invalid state in the S - R latch.




Gated D Latch

- When EN is HIGH,
 - ❖ $D=HIGH \rightarrow$ latch is SET
 - ❖ $D=LOW \rightarrow$ latch is RESET
- Hence when EN is HIGH, Q ‘follows’ the D (data) input.
- Characteristic table:

| EN | D | $Q(t+1)$ | |
|------|-----|----------|-----------|
| 1 | 0 | 0 | Reset |
| 1 | 1 | 1 | Set |
| 0 | X | $Q(t)$ | No change |

When $EN=1$, $Q(t+1) = D$

Transparent D-Latch

 


| EN | D | Q | \overline{Q} |
|----|---|-------|------------------|
| 0 | X | Q_0 | \overline{Q}_0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

EN: Enable

D Latch

- Two inputs: CLK , D
 - CLK : controls *when* the output changes
 - D (the data input): controls *what* the output changes to
- Function
 - When $CLK = 1$,
 D passes through to Q (*transparent*)
 - When $CLK = 0$,
 Q holds its previous value (*opaque*)
- Avoids invalid case when
 $Q \neq \text{NOT } \overline{Q}$

D Latch
Symbol

 


Latch Circuits: Not Suitable

- Latch circuits are not suitable in synchronous logic circuits.
- When the enable signal is active, the excitation inputs are gated directly to the output Q .
- Thus, any change in the excitation input immediately causes a change in the latch output.


Edge-Triggered Flip-flops

 - *Flip-flops*: synchronous bistable devices
- Output changes state at a specified point on a triggering input called the *clock*.
- Change state either at the *positive edge* (rising edge) or at the *negative edge* (falling edge) of the clock signal.



Clock Edges




Positive Edge Transition

 




Negative Edge Transition

Edge-Triggered Flip-flops

   - S-R, D and J-K edge-triggered flip-flops. Note the “>” symbol at the clock input.



Positive edge-triggered flip-flops

   

Negative edge-triggered flip-flops

S-R Flip-flop

- **S-R flip-flop:** on the triggering edge of the clock pulse,
 - ❖ $S=\text{HIGH}$ (and $R=\text{LOW}$) a SET state
 - ❖ $R=\text{HIGH}$ (and $S=\text{LOW}$) a RESET state
 - ❖ both inputs LOW a no change
 - ❖ both inputs HIGH a invalid

■ Characteristic table of positive edge-triggered S-R flip-flop:

| <i>S</i> | <i>R</i> | <i>CLK</i> | <i>Q(t+1)</i> | Comments |
|-----------------|-----------------|-------------------|----------------------|------------------|
| 0 | 0 | X | <i>Q(t)</i> | No change |
| 0 | 1 | ↑ | 0 | Reset |
| 1 | 0 | ↑ | 1 | Set |
| 1 | 1 | ↑ | ? | Invalid |

X = irrelevant (“don’t care”)


↑ = clock transition LOW to HIGH

S-R Flip-flop

- It comprises 3 parts:
 - ❖ a basic *NAND latch*
 - ❖ a *pulse-steering* circuit
 - ❖ a *pulse transition detector* (or *edge detector*) circuit
- The **pulse transition detector** detects a rising (or falling) edge and produces a very *short-duration spike*.

S-R Flip-flop

The pulse transition detector.

 

D Flip-flop


- **D flip-flop**: single input D (data)

- ❖ D =HIGH a SET state

- ❖ D =LOW a RESET state

- Q follows D at the clock edge.

 - Convert S-R flip-flop into a D flip-flop: add an inverter.



A positive edge-triggered D flip-flop formed with an S-R flip-flop.

| <i>D</i> | <i>CLK</i> | $Q(t+1)$ | Comments |
|----------|------------|----------|----------|
| 1 | ↑ | 1 | Set |
| 0 | ↑ | 0 | Reset |


↑ = clock transition LOW to HIGH

J-K Flip-flop

- J-K flip-flop: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a *toggle* state.
 - ❖ $J=\text{HIGH}$ (and $K=\text{LOW}$) a SET state
 - ❖ $K=\text{HIGH}$ (and $J=\text{LOW}$) a RESET state
 - ❖ both inputs LOW a no change
 - ❖ both inputs HIGH a toggle

J-K Flip-flop

■ J-K flip-flop.

 


■ Characteristic table.

| <i>J</i> | <i>K</i> | <i>CLK</i> | $Q(t+1)$ | Comments |
|----------|----------|------------|----------|-----------|
| 0 | 0 | ↑ | $Q(t)$ | No change |
| 0 | 1 | ↑ | 0 | Reset |
| 1 | 0 | ↑ | 1 | Set |
| 1 | 1 | ↑ | $Q(t)'$ | Toggle |

$$Q(t+1) = J.Q' + K'.Q$$


| <i>Q</i> | <i>J</i> | <i>K</i> | $Q(t+1)$ |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

D Flip-Flop: PR & CLR Timing

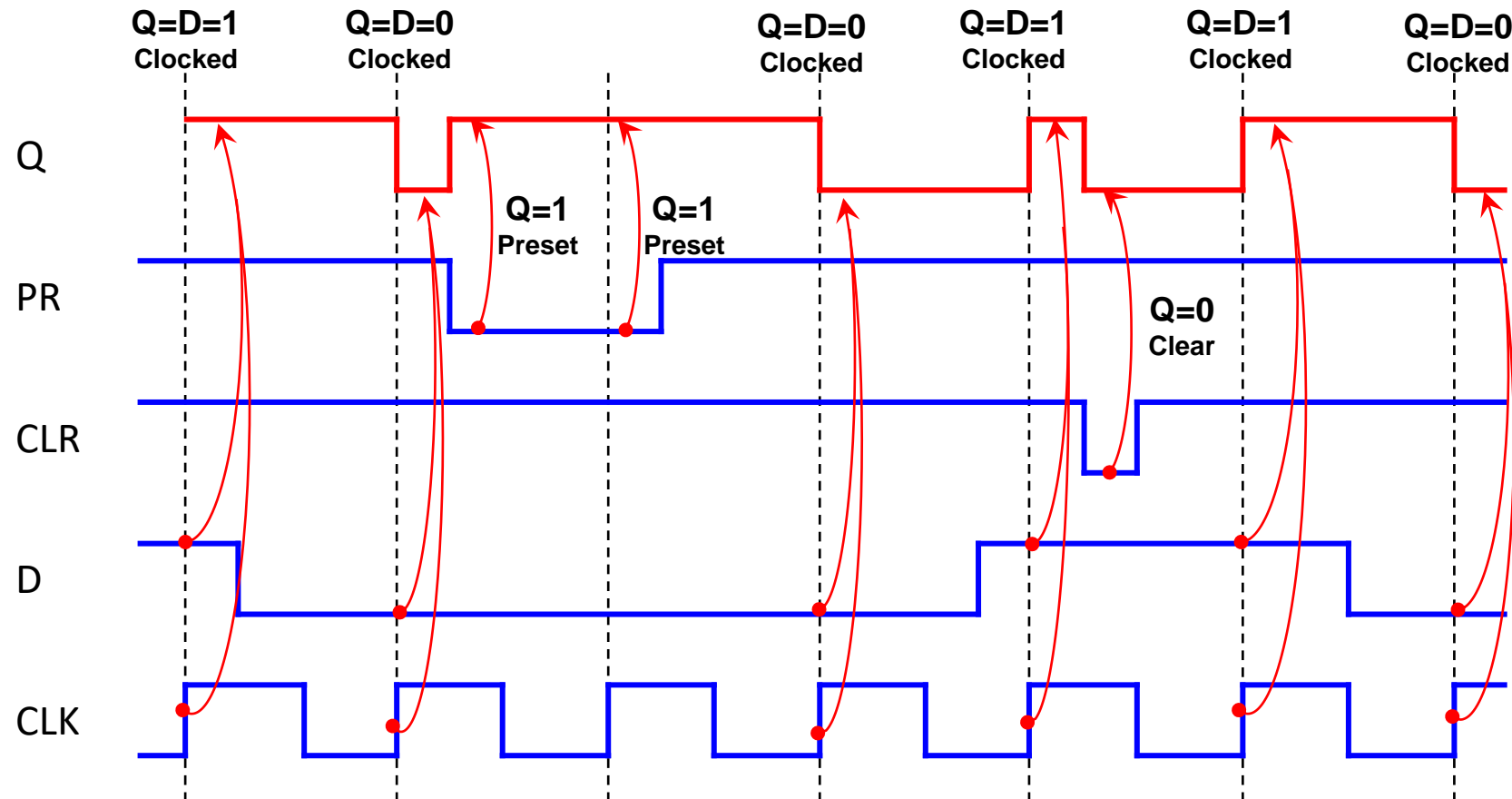


D Flip-Flop

 - **Inputs:** CLK , D
- **Function**
 - Samples D on rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK
- Called *edge-triggered*
- Activated on the clock edge




D Flip-Flop: Excitation Table

 


| D | CLK | Q | \bar{Q} |
|---|-----|---|-----------|
| 0 | ↑ | 0 | 1 |
| 1 | ↑ | 1 | 0 |

↑ : Rising Edge of Clock




Transparent D-Latch: Example Timing

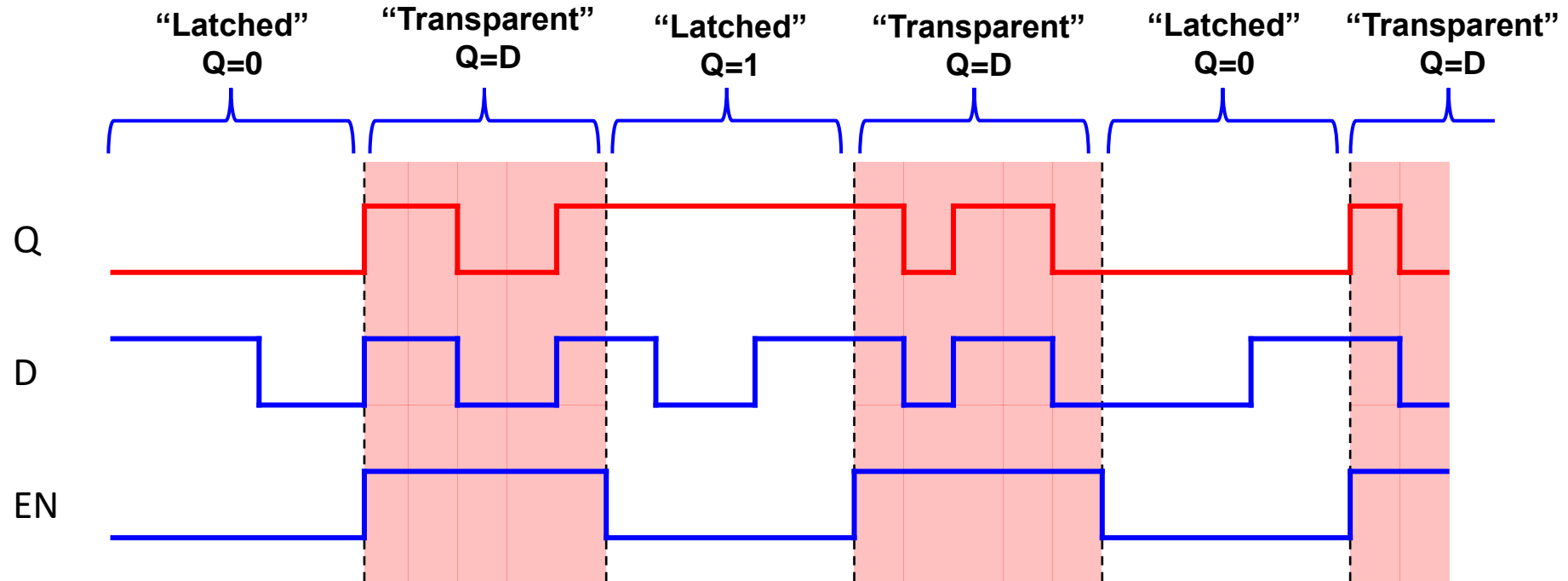

D Flip-Flop: Example Timing


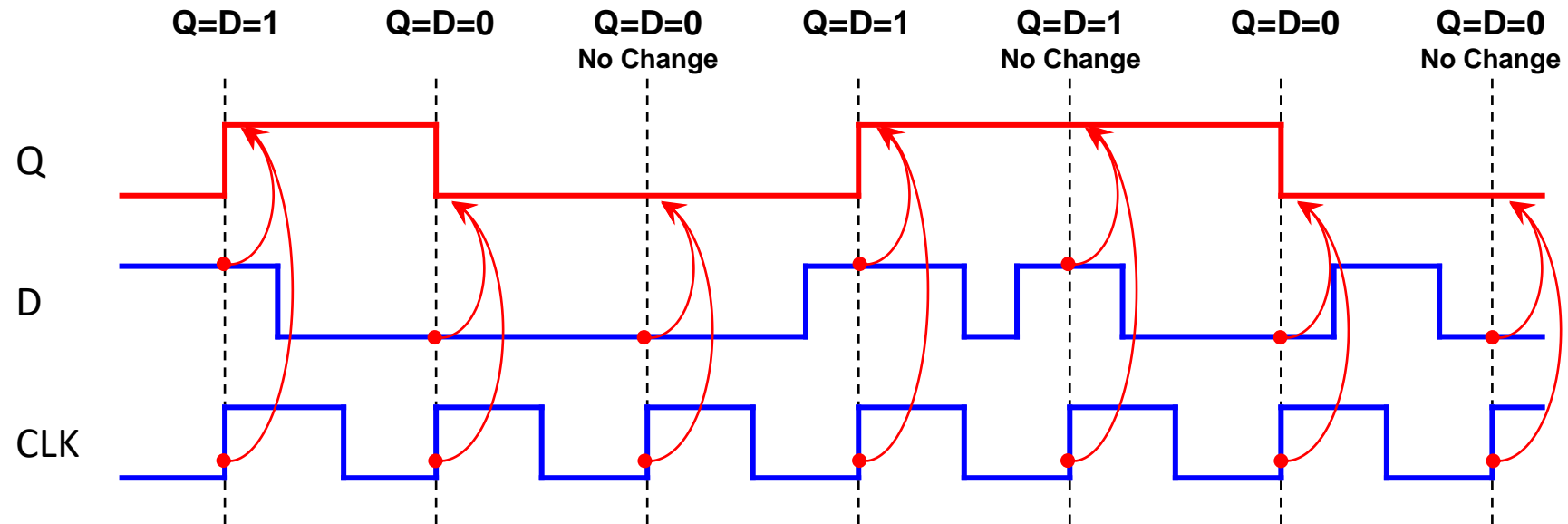


D Latch vs. D Flip-Flop

   

T Flip-flop

 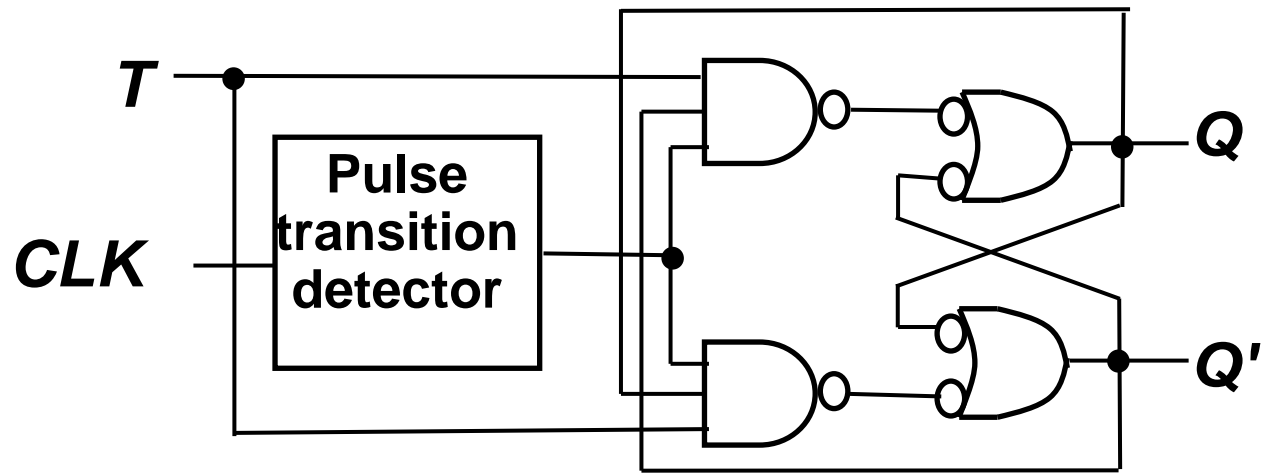- **T flip-flop**: single-input version of the J-K flip flop, formed by tying both inputs together.




■ Characteristic table.

| T | CLK | $Q(t+1)$ | Comments |
|-----|-------|----------|-----------|
| 0 | ↑ | $Q(t)$ | No change |
| 1 | ↑ | $Q(t)'$ | Toggle |


$$Q(t+1) = T.Q' + T'.Q$$

| Q | T | $Q(t+1)$ |
|-----|-----|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Sequential Logic & The Flip-Flop

 

J/K Flip-Flop: Excitation Table

 

| J | K | CLK | Q |
|---|---|-----|-------------|
| 0 | 0 | ↑ | Q_0 |
| 0 | 1 | ↑ | 0 |
| 1 | 0 | ↑ | 1 |
| 1 | 1 | ↑ | \bar{Q}_0 |

No Change

Clear


Set

Toggle

↑ : Rising Edge of Clock


\bar{Q} : Complement of Q

J/K Flip-Flop: Example Timing

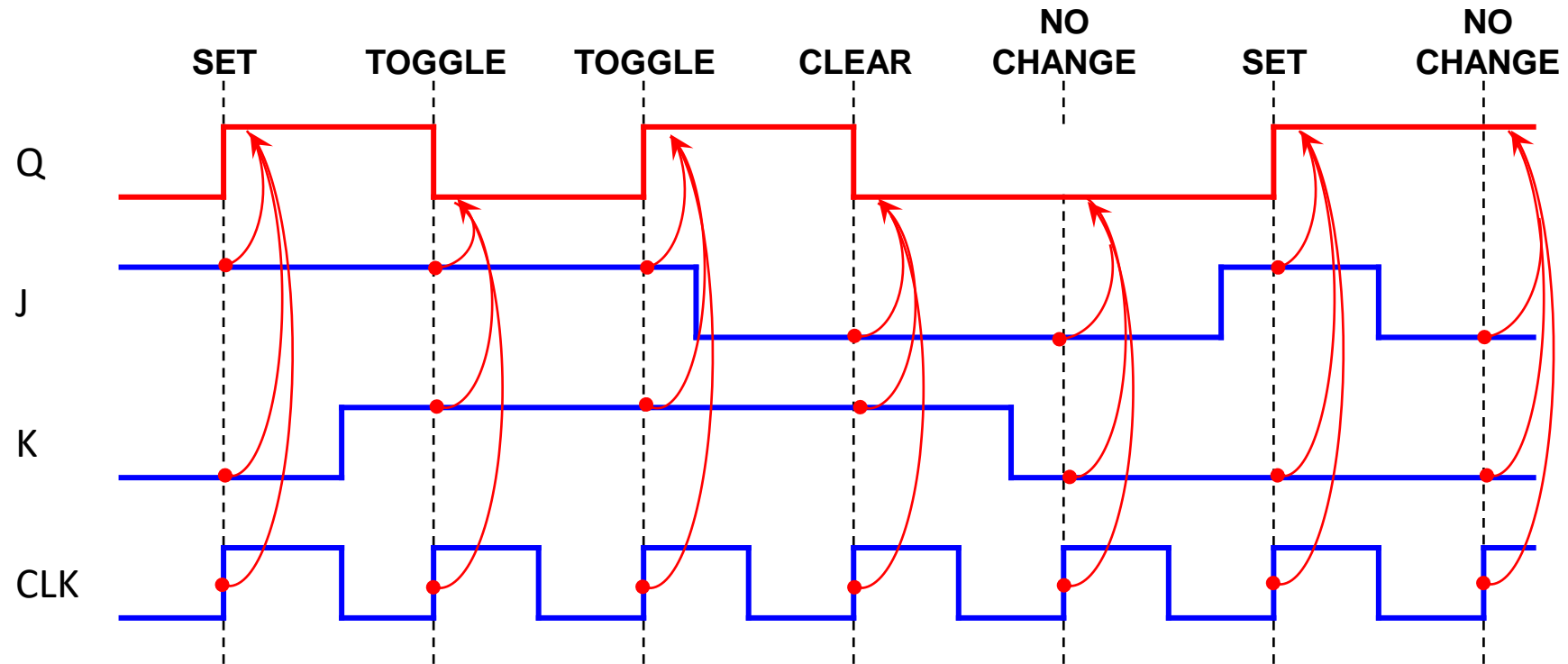

POS & NEG Edge Triggered D


Positive Edge Trigger

 

| D | CLK | Q | \overline{Q} |
|---|-----|---|----------------|
| 0 | ↑ | 0 | 1 |
| 1 | ↑ | 1 | 0 |

↑ : Rising Edge of Clock

Negative Edge Trigger

 


| D | CLK | Q | \overline{Q} |
|---|-----|---|----------------|
| 0 | ↓ | 0 | 1 |
| 1 | ↓ | 1 | 0 |

↓ : Falling Edge of Clock

POS & NEG Edge Triggered J/K


Positive Edge Trigger

 

| J | K | CLK | Q |
|---|---|-----|------------------|
| 0 | 0 | ↑ | Q_0 |
| 0 | 1 | ↑ | 0 |
| 1 | 0 | ↑ | 1 |
| 1 | 1 | ↑ | $\overline{Q_0}$ |

↑ : Rising Edge of Clock

Negative Edge Trigger

 

| J | K | CLK | Q |
|---|---|-----|------------------|
| 0 | 0 | ↓ | Q_0 |
| 0 | 1 | ↓ | 0 |
| 1 | 0 | ↓ | 1 |
| 1 | 1 | ↓ | $\overline{Q_0}$ |

↓ : Rising Edge of Clock

Asynchronous Inputs

Asynchronous inputs (Preset & Clear) are used to override the clock/data inputs and force the outputs to a predefined state.

The Preset (PR) input forces the output to:

$$Q = 1 \text{ \& } \overline{Q} = 0$$

The Clear (CLR) input forces the output to:


$$Q = 0 \text{ \& } \overline{Q} = 1$$

| PR PRESET | CLR CLEAR | CLK CLOCK | D DATA | Q | \overline{Q} |
|--------------|--------------|--------------|-----------|---|----------------|
| 1 | 1 | ↑ | 0 | 0 | 1 |
| 1 | 1 | ↑ | 1 | 1 | 0 |
| 0 | 1 | X | X | 1 | 0 |
| 1 | 0 | X | X | 0 | 1 |
| 0 | 0 | X | X | 1 | 1 |

Asynchronous Preset

Asynchronous Clear

ILLEGAL CONDITION

 

Flip-Flop Vs. Latch

- The primary difference between a D flip-flop and D latch is the EN/CLOCK input.
- The flip-flop's CLOCK input is edge sensitive, meaning the flip-flop's output changes on the edge (rising or falling) of the CLOCK input.
- The latch's EN input is level sensitive, meaning the latch's output changes on the level (high or low) of the EN input.