

Flip flop is at 'set' state when outputs Q and Q' are respectively

- a) 1 and 0      b) 0 and 1      c) 1 and 1      d) 0 and 0

D flip flop contains output that are

- a) complement      b) similar      c) infinite      d) zero

D flip flop contains----- clock input(s)

- a) one      b) two      c) three      d) four

Flip flop is at 'reset' state when outputs Q and Q' are respectively

- a) 1 and 0      b) 0 and 1      c) 1 and 1      d) 0 and 0

Sequential circuits require a

- a) timing motors      b) timing transformers      c) timing generators      d) timing flips

Circuit which has a feedback is

- a) combinational circuit      b) sequential circuit      c) systematic circuit      d) correctional circuit

Circuit which has two stable states are termed as

- a) combinational circuit      b) bistable circuits      c) unit stable circuits      d) tri stable circuits

Flip flop is considered set when it stores

- a) logic 1      b) logic x      c) logic z      d) logic 0

If we don't want to change the state of SR flip flop, S and R must be

- a) 1 and 0 respectively      b) 0 and 1 respectively      c) 1 and 1 respectively      d) 0 and 0 respectively

Logic circuits which don't have memory are

- a) combinational circuit      b) sequential circuit      c) systematic circuit      d) correctional circuit

Logic circuits that incorporate memory are called

- a) combinational circuit      b) sequential circuit      c) systematic circuit      d) correctional circuit

The term hold always means \_\_\_\_\_.

- a)  $Q = 0, \bar{Q} = 1$       b)  $Q = 1, \bar{Q} = 0$       c)  $Q = 0, \bar{Q} = 0$       d) no change

The signal used to identify edge-triggered flip-flops is \_\_\_\_\_.

- a) a bubble on the clock input      an inverted "L" on the output  
the letter "E" on the enable input      a triangle on the clock input

Whose operations are more faster among the following?

- a) Combinational circuits      b) Sequential circuits      c) Latches      d) Flip-flops

What is a trigger pulse?

- a) A pulse that starts a cycle of operation      b) A pulse that reverses the cycle of operation  
c) A pulse that prevents a cycle of operation      d) A pulse that enhances a cycle of operation

Sequential circuits require a

- a) timing motors      b) timing transformers      c) timing generators      d) timing flips

When the output of the NOR gate S-R flip-flop is in the HOLD state (no change), the inputs are \_\_\_\_\_.

- a)  $S = 1, R = 1$       b)  $S = 1, R = 0$       c)  $S = 0, R = 1$       d)  $S = 0, R = 0$

The result " $X + XY = X$ " follows which of these laws?

- a) Consensus law      b) Distributive law      c) Duality law      d) Absorption law

Which of the following options represent the correct reduction of  $XYZ + \bar{X}YZ$  ?

- a) 0      b) YZ      c)  $X + X$       b) 2YZ

The following hexadecimal number (1E.43)<sub>16</sub> is equivalent to

- (36.506)<sub>8</sub>      (36.206)<sub>8</sub>      (35.506)<sub>8</sub>      (35.206)<sub>8</sub>

4) How many entries will be in the truth table of a 4-input NAND gate?

- 6      8      32      16

Convert the binary number 1001.0010<sub>2</sub> to decimal

- a) 90.125      b) 9.125      c) 125      d) 12.5

Convert hexadecimal value C1 to binary

a) 11000001

b) 1000111

c) 111000100

d) 111000001

Convert the octal number  $17_8$  to decimal

a) 51

b) 82

c) 57

d) 15

Convert the binary number  $010111100_2$  to octal.

a)  $172_8$

b)  $272_8$

c)  $174_8$

d)  $274_8$

1's complement of 1011001 is

0100111

0101100

0100110

0110110

2's complement of 1011011 is

0100011

0110101

0100011

0100101

The output of a NOR gate is HIGH if \_\_\_\_\_.

a) all inputs are HIGH

b) any input is HIGH

c) any input is HIGH

d) all

inputs are LOW

The format used to present the logic output for the various combinations of logic inputs to a gate is called a(n):

Boolean constant

Boolean variable

truth table

input logic function

The Boolean expression for a 3-input AND gate is \_\_\_\_\_.

$X = AB$

$X = ABC$

$X = AB + C$

$X = A + B + C$

If the input to a NOT gate is A and the output is X, then \_\_\_\_\_.

$X = A$

$X = 0$

$X = \bar{A}$

none of them

The expressions,  $\overline{A \cdot B} = \bar{A} + \bar{B}$ , are equivalent

True

False

Subtraction is commutative.

True

False

The OR function is Boolean multiplication and the AND function is Boolean addition.

True

False

In Boolean algebra,  $A + 1 = 1$ .

True

False

The product-of-sums (POS) is basically the ORing of ANDed terms.

A flip-flop is in the CLEAR condition when  $Q = 1, \bar{Q} = 1$ .

a) True

b) False

Some flip-flops have invalid states

a) True

b) False

When the output of the NOR gate S-R flip-flop is  $Q = 1$  and  $\bar{Q} = 0$ , the inputs are  $S = 1, R = 1$ .

a) True

b) False

A TOGGLE input to a J-K flip-flop causes the Q and  $\bar{Q}$  outputs to switch to their opposite state.

a) True

b) False

Edge-triggered flip-flops can be identified by the triangle on the clock input.

a) True

b) False